

49:1 UNUN Transformer Designs

Jacques Audet
Oct. 2023

49 to 1 Standard UNUN (FT240-43) Tap at two turns

Measurement SET-UP

Compensation capacitors will be added at the simulation stage

NO need to use a dual winding primary/secondary. A tapped single winding will improve coupling slightly as shown by simulations and simplify construction

2390 Ω total load simulates antenna resistance and allows verification of Input VSWR

FT240-43 X2 cores
14 Turns total
Initial permeability = 850

16 wire

OUT
To VNA

IN


Tap at 2 turns

Measured Coupling coeff. = 0.99
Primary $L_p = 16.55 \mu\text{H}$
Ref: Inductors M and K Calculations.xls

All transmission tests done with HP8753D VNA, using full two port calibration.

Added 150 pF Cap across input
optimizes VSWR and losses above 10 MHz
The measured primary inductance of 16.55 μ H
improves SWR below 3 MHz, but losses are still high.

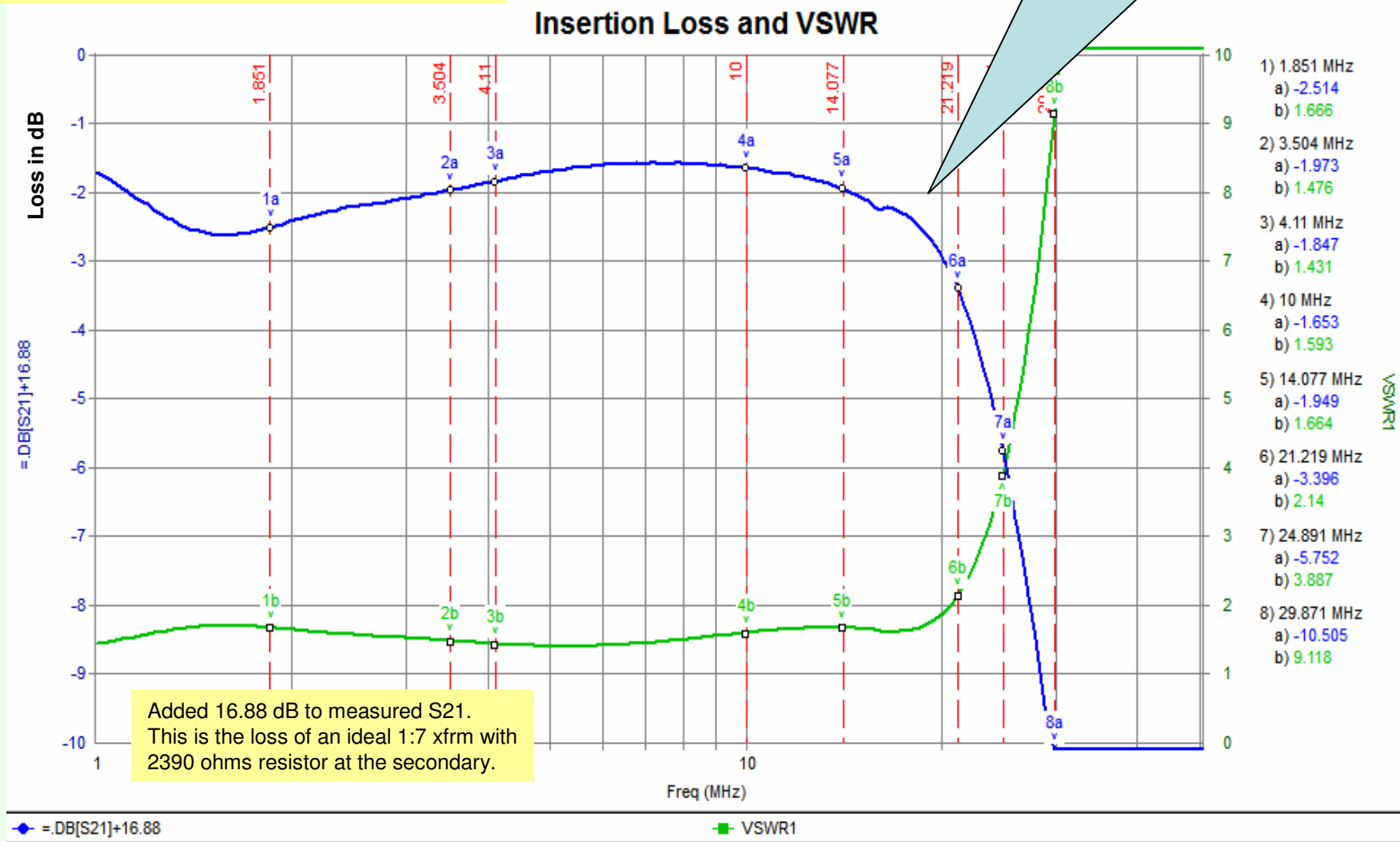FT240-43 gives high insertion loss, at least with
2 to 14 turns.
BUT VSWR is low (1.4 to 2.0) from 1 to 20 MHz
even with coupling coeff = 0.99



MEASURED RESPONSE

FAIR-RITE FT140-43


Fair-Rite calls it an 'inductive component'

68 pF in shunt on primary
3900 pF in series

Max power: one core, 2 pri. turns = 12W @ 3.5 MHz,
Max power: two cores, 3 pri. turns = 104W @ 3.5 MHz



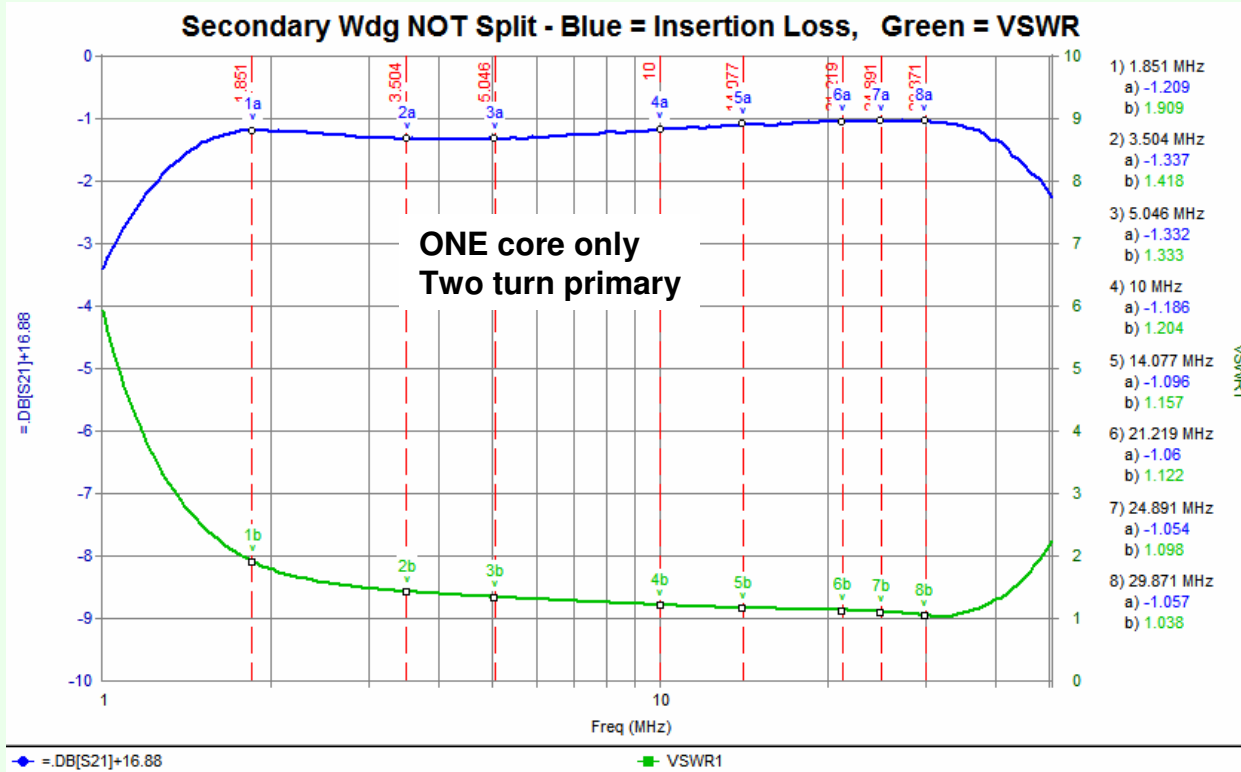Fair-Rite core
5943002701
1.4 x 0.906 x 0.5 in.
43 material $\mu = 800$




Too much losses at
both low and high
frequencies

Not Recommended !

Ref: UNUN 49to1-1cores-26wire-14a2Tours-NoSplitSecondary-FT140-43.wsp

Circuit used for Simulations

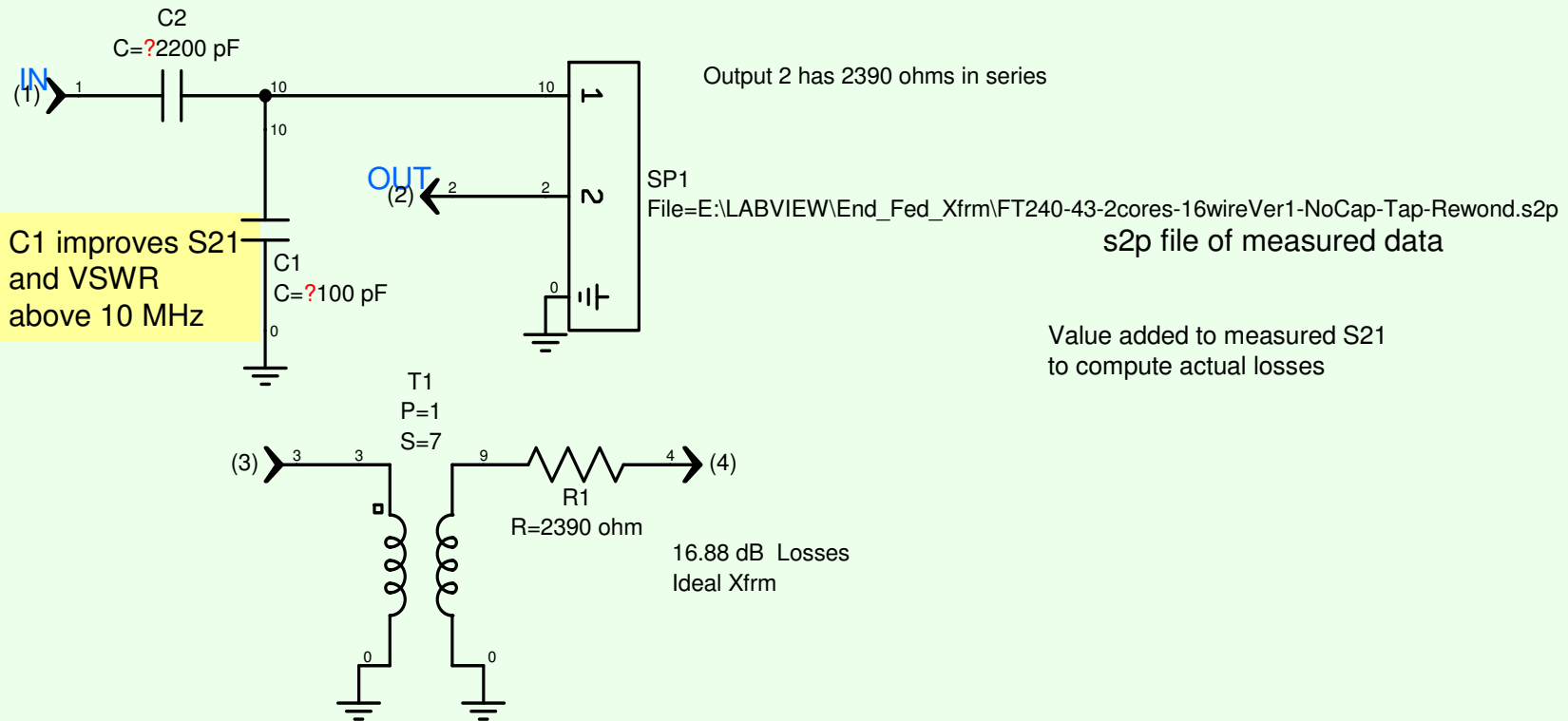
Improving VSWR and losses at the low frequencies.
C2's reactance cancels the primary inductance.



49 to 1 Standard UNUN # 16 wire separate primary/secondary


FT240-52 X2 cores 2/14 turns

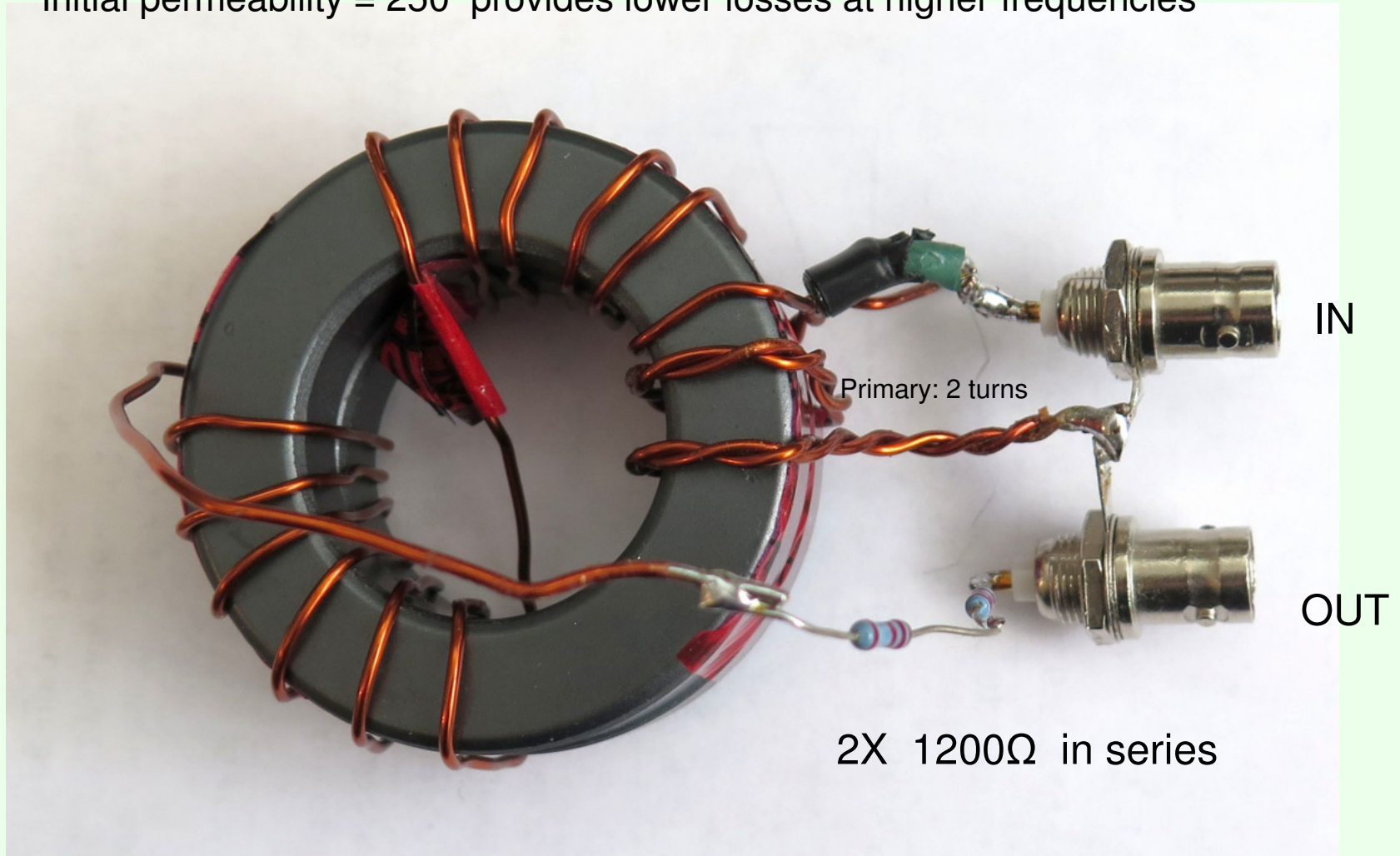Initial permeability = 250 provides lower losses at higher frequencies




Added 69 pF cap. across input and
2200 pF in series with the input

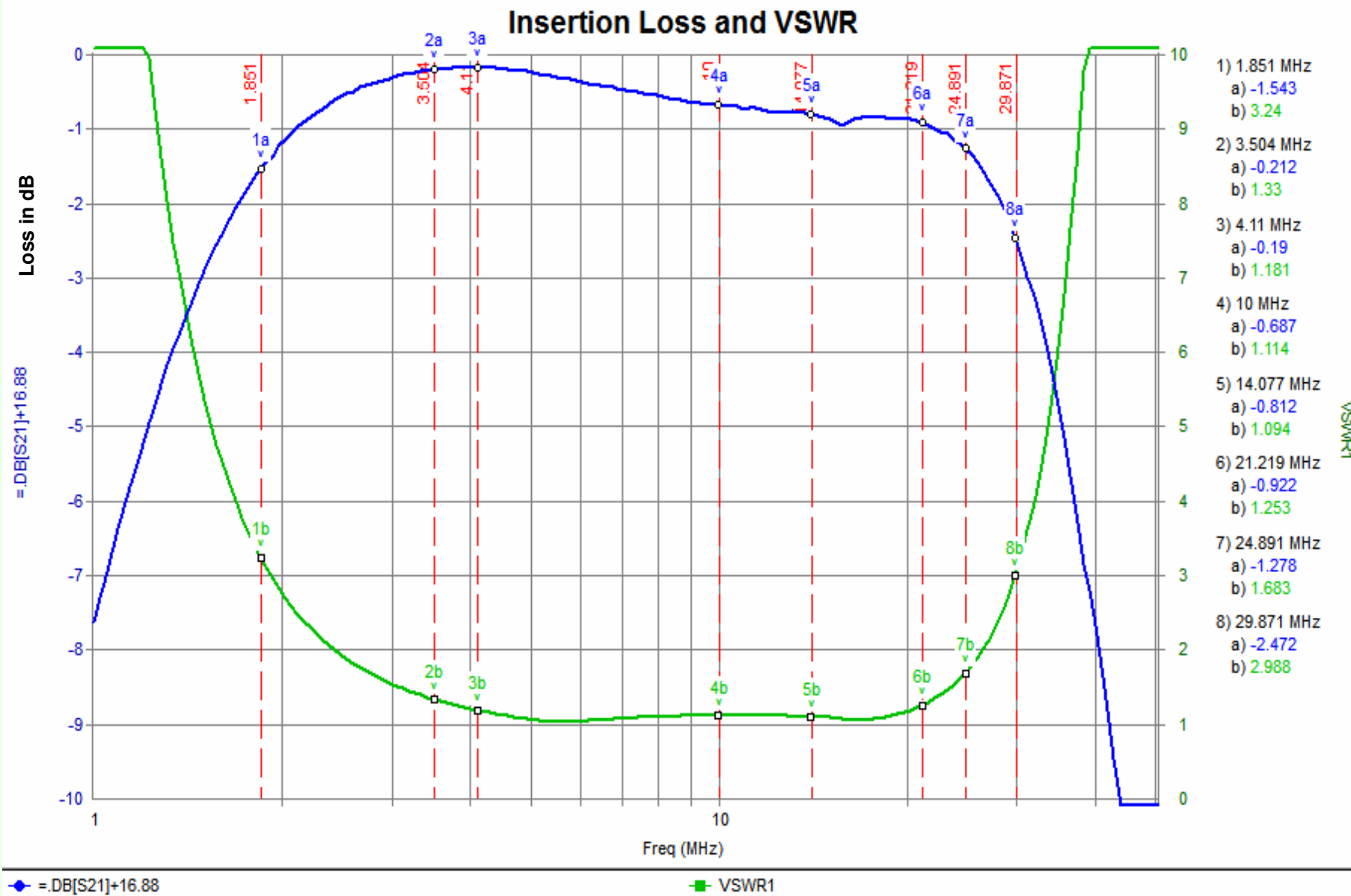FT240-52 gives much lower insertion loss
at least with 2 to 14 turns.



49 to 1 Auto Transformer 140 mil wide Cu strip on primary, # 26 wire secondary


FT240-52 X2 cores

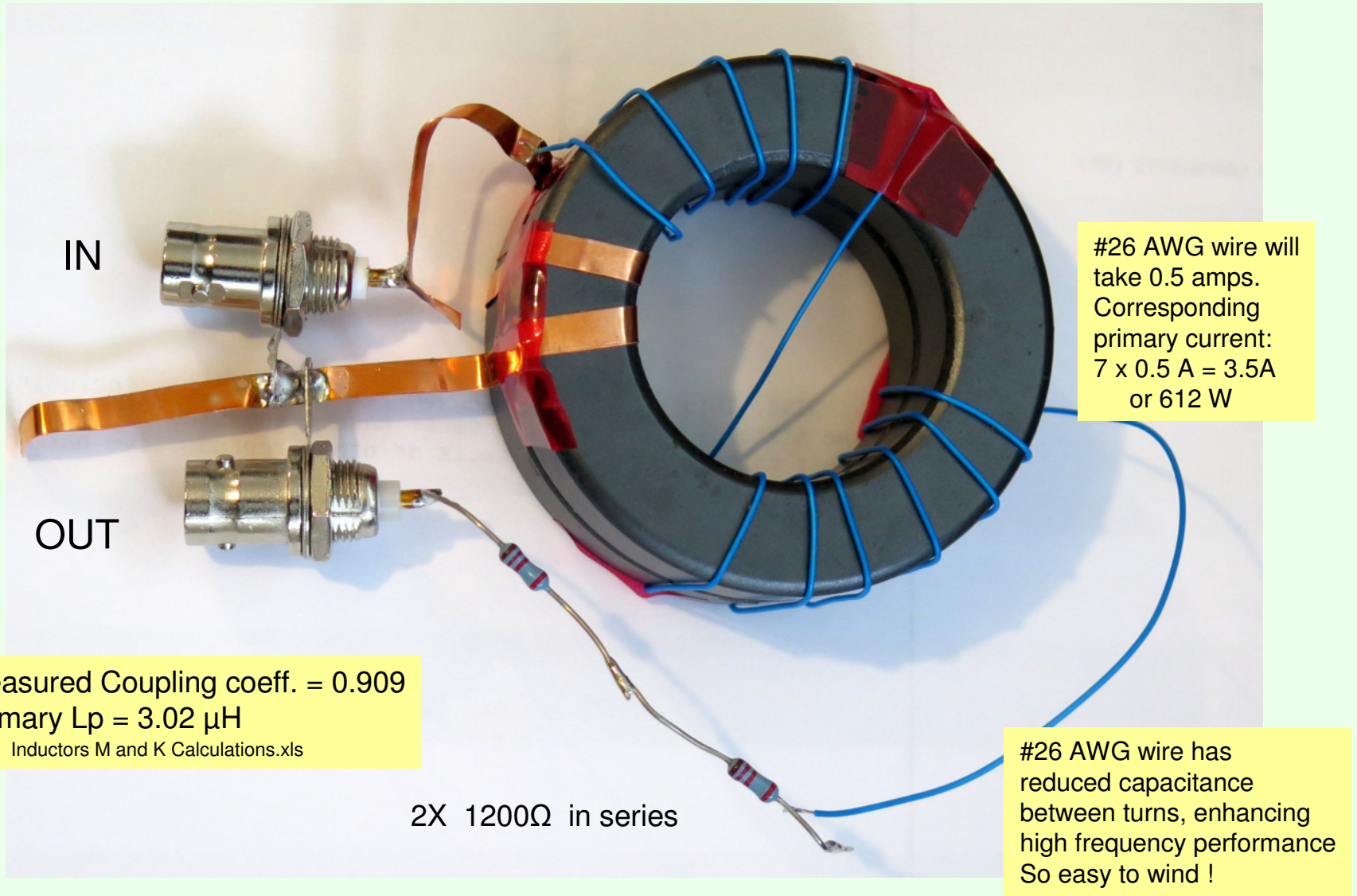

Ref: Unun-1 to7-TransformerFT240-52_26wire-Ver2.wsp


Added 88 pF Cap across input and
2200 pF in series with the input

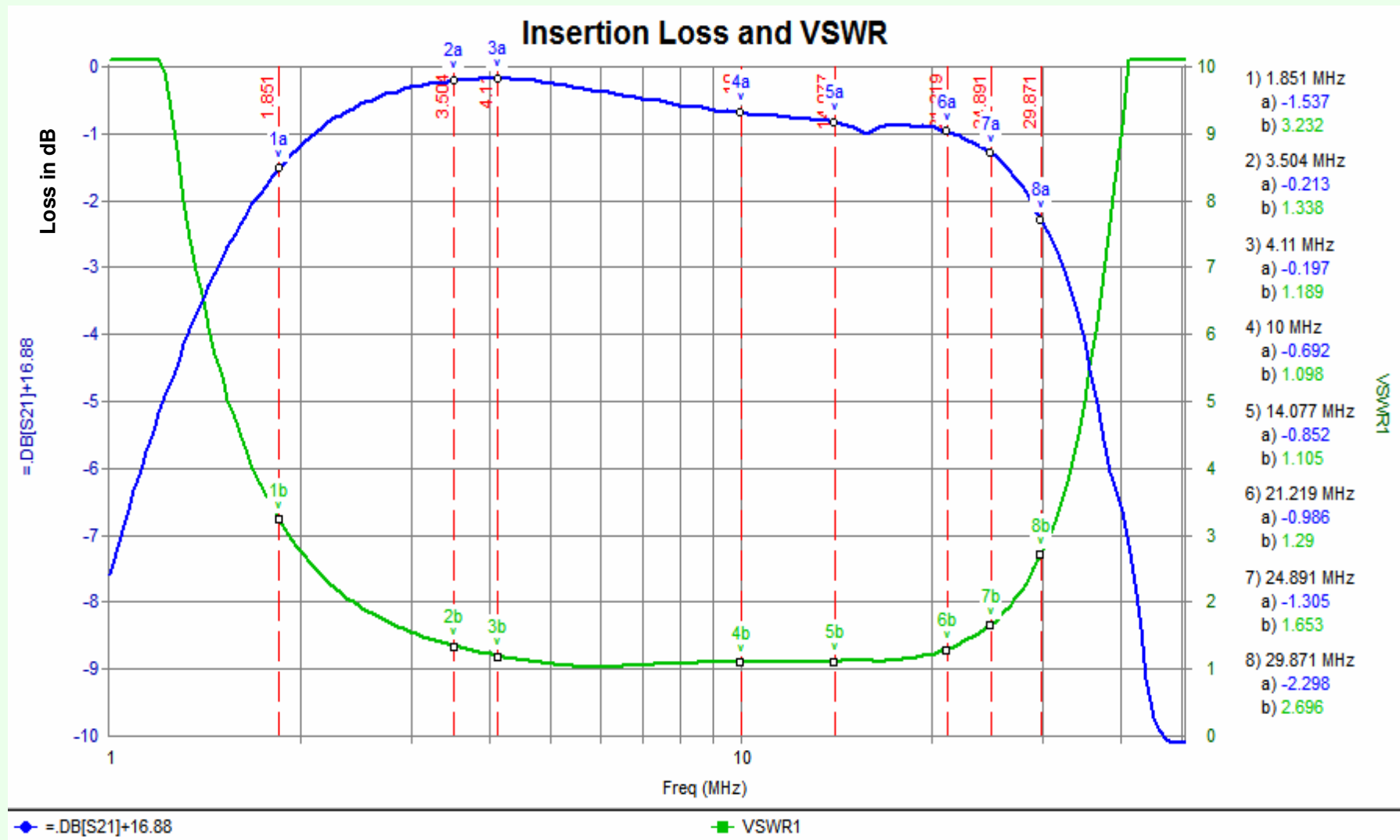Coupling coeff. K is too low = 0.909
Attenuation above 20 MHz increases.






Ref: Unun-1 to7-TransformerFT240-52_26wire-Ver2.wsp

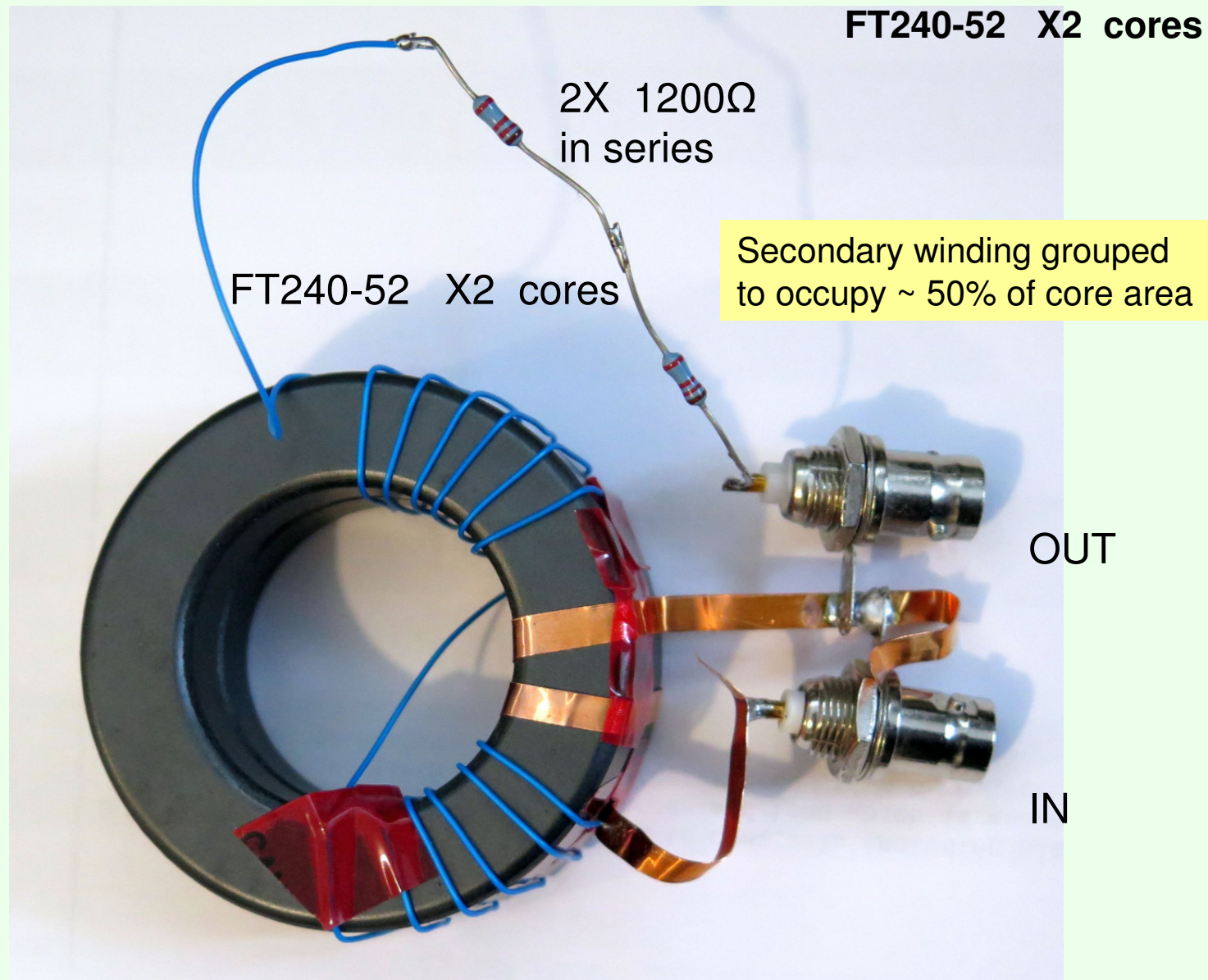
49 to 1 Auto Transformer 140 mil wide Cu strip on primary, # 26 wire secondary



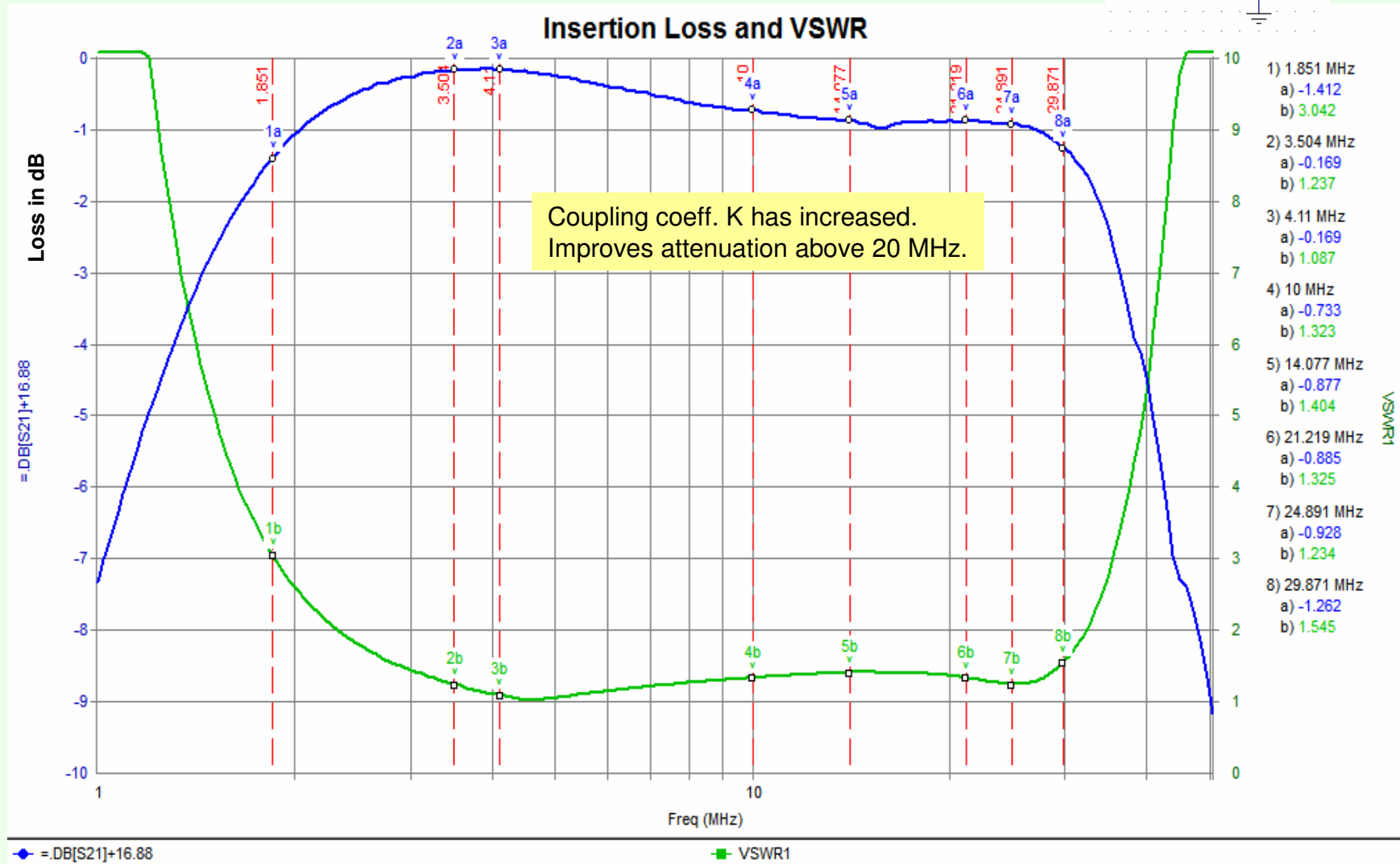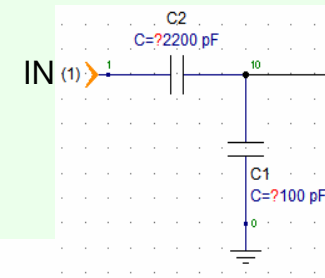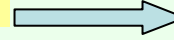
Added 100 pF Cap across input and 2200 pF in series with the input



EFFECT of Series Capacitor at input


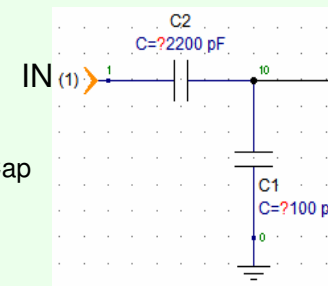


Added 100 pF Cap
across input

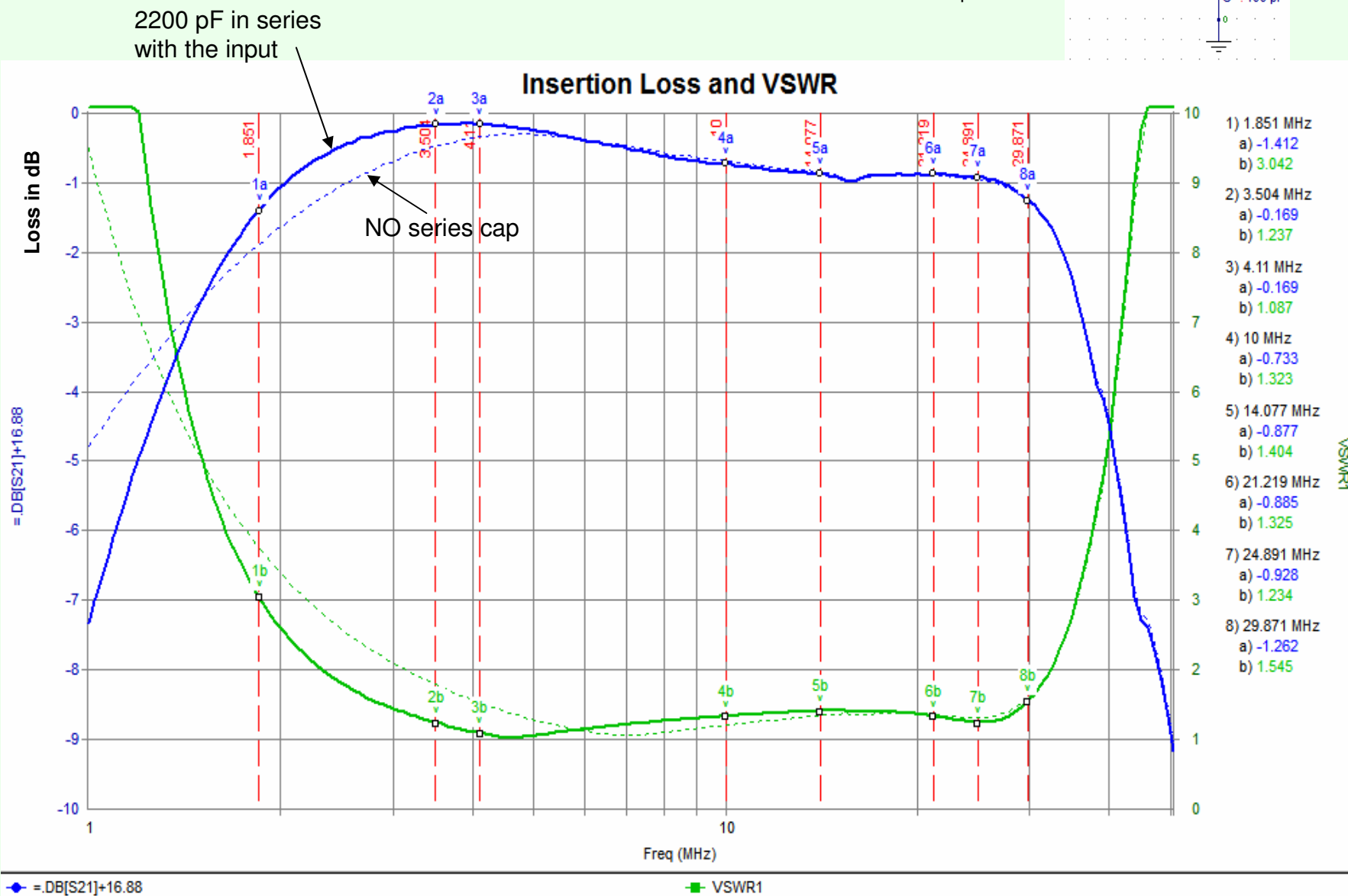


Improving performance on 160m.

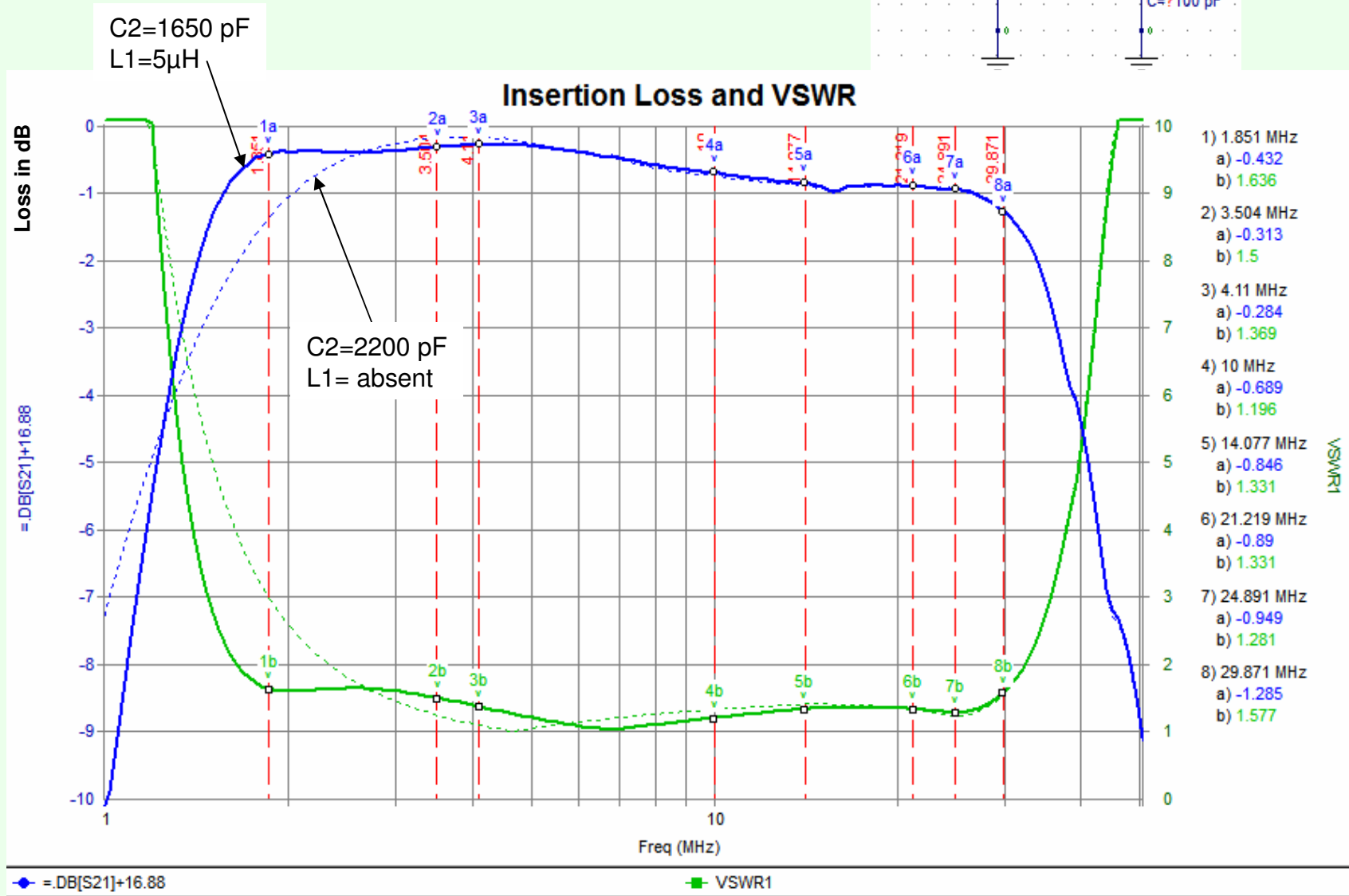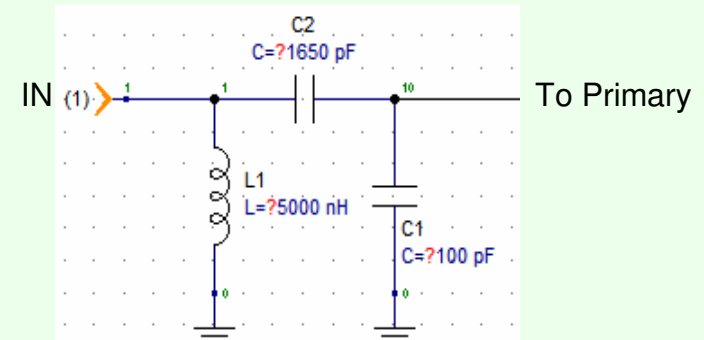Added shunt $5\mu\text{H}$ Inductor + 1650 pF in series with the input



49 to 1 Auto Transformer 140 mil wide Cu strip on primary, # 26 wire secondary

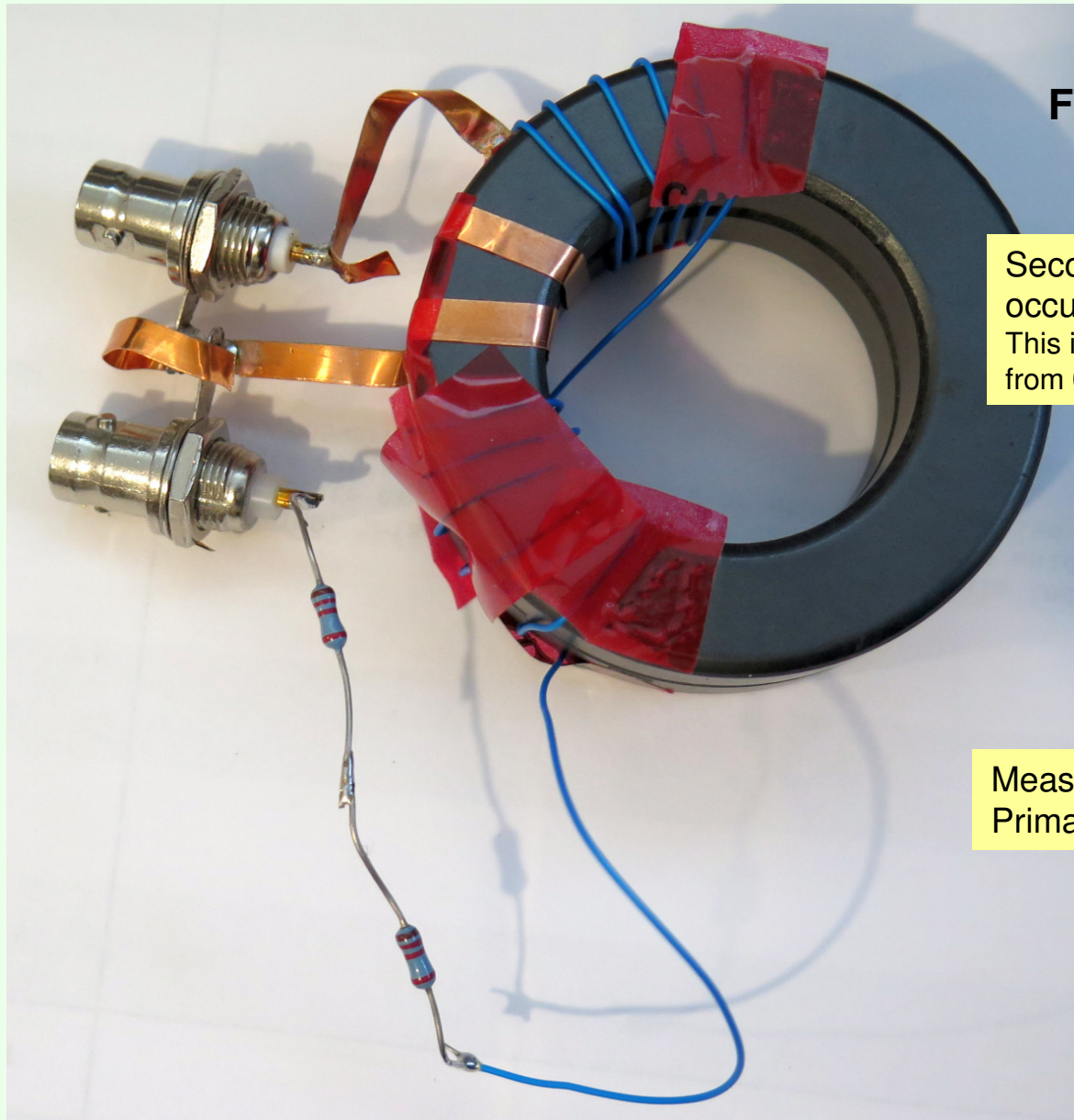


FT240-52 X2 cores

Secondary winding grouped to occupy ~ 40% of area.
This increased the coupling coeff. from 0.909 to 0.928 (See slide 6)

Measured Coupling coeff. = 0.928
Primary Inductance = 3.03 μH

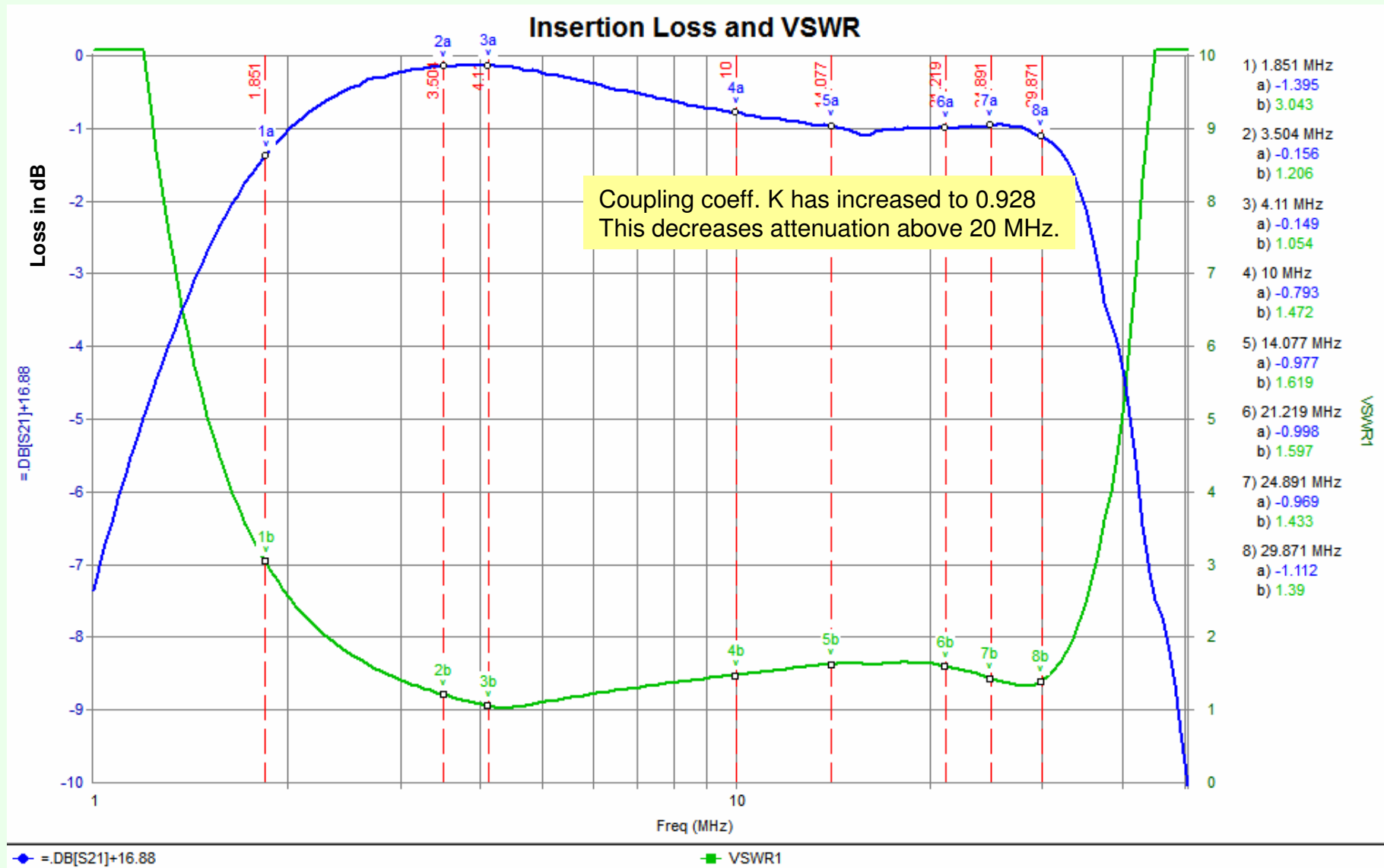Added 112 pF Cap across input and
2200 pF in series with the input



Ref: FT240-52-2cores-26wireVer2-NoCap-Tap-WdgsTighter.wsp

49 to 1 Auto Transformer 140 mil wide Cu strip on primary, # 26 wire secondary

FT240-52 X2 cores


Tape added on last 7 turns



Secondary winding grouped to occupy ~ 35% of area. This increased the coupling coeff. from 0.909 to 0.938 (See slide 6)

Measured Coupling coeff. = 0.938
Primary Inductance = 3.0 μ H

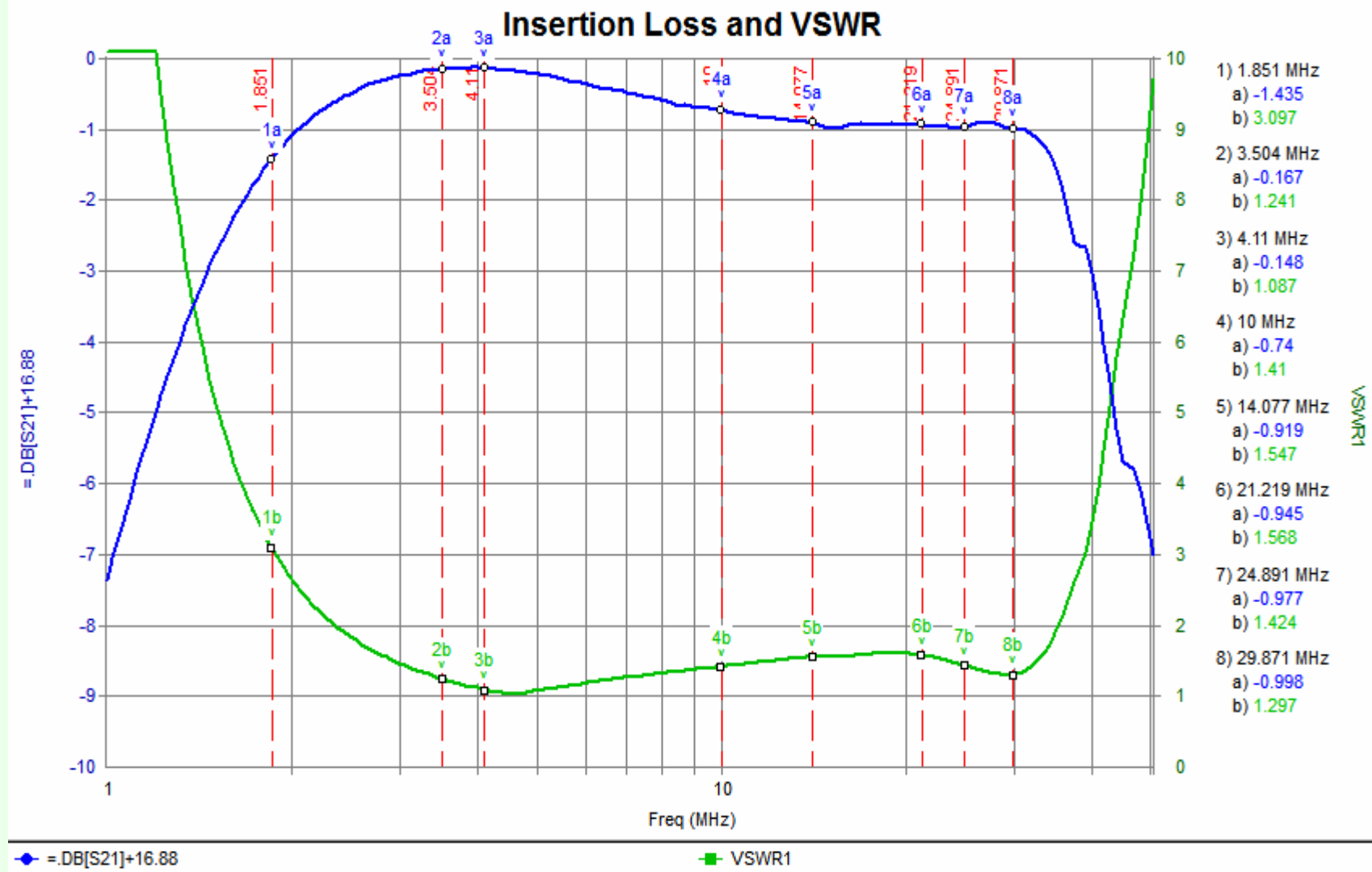Added 100 pF Cap across input and
2200 pF in series with the input




Ref: FT240-52-2cores-26wireVer2-NoCap-Tap-WdgsTighter-TapeLast7T.wsp

49 to 1 Auto Transformer 140 mil wide Cu strip on primary, # 26 wire secondary

FT240-52 X2 cores

Tape added on last 7 turns

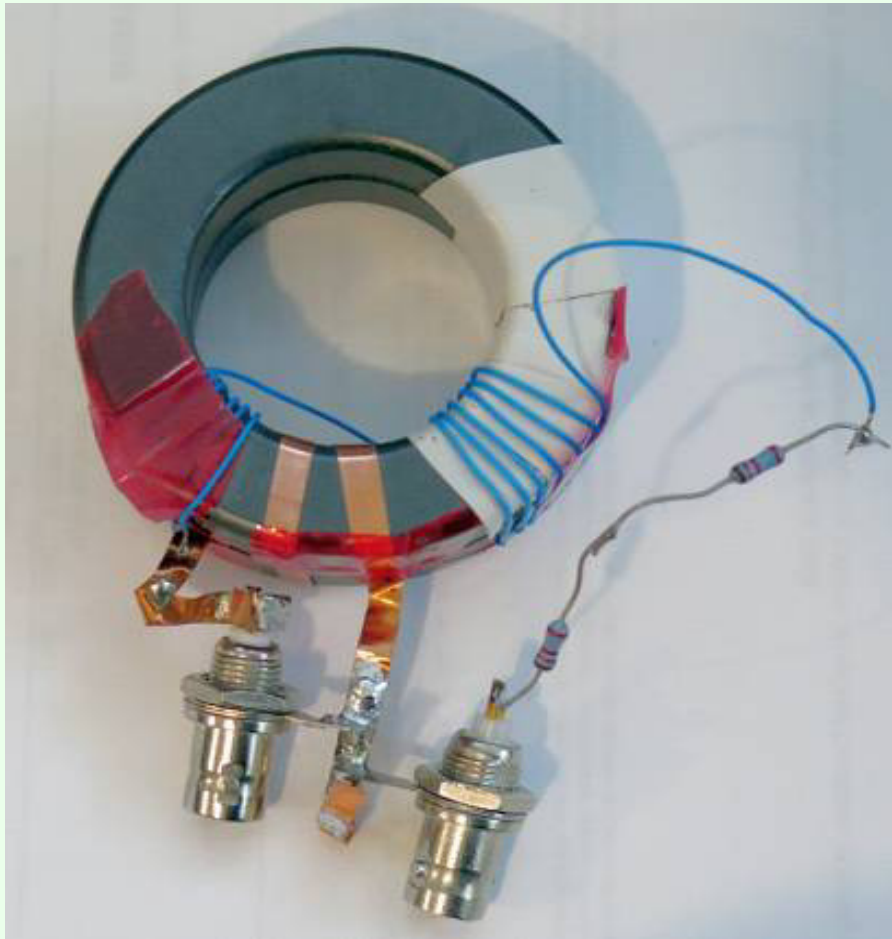


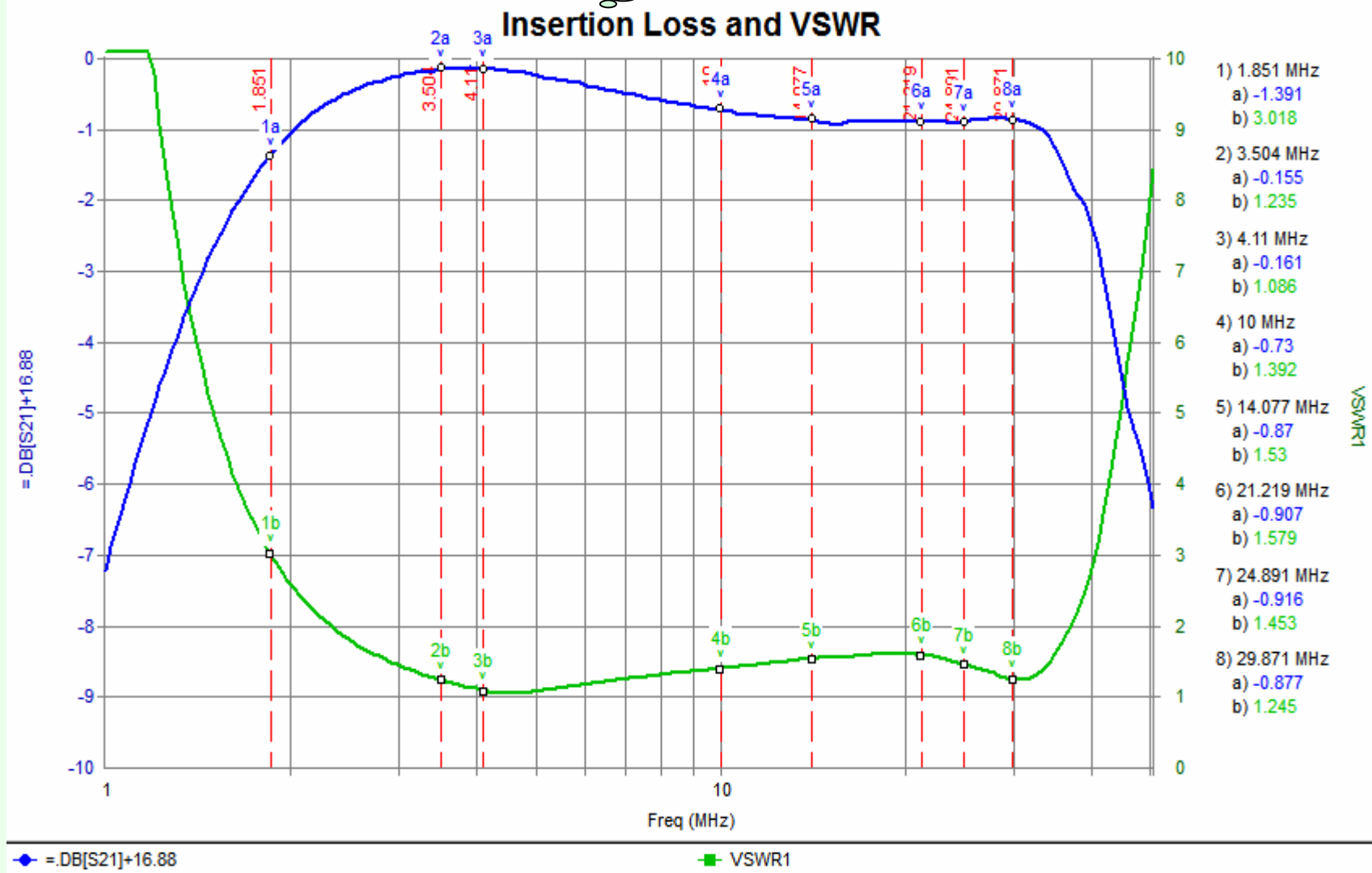
Secondary winding grouped to occupy ~ 30% of area.
This increased the coupling coeff. from 0.909 to 0.957 (See slide 6)

Measured Coupling coeff. = 0.957
Primary Inductance = 3.12 μ H

Added 100 pF Cap across input and
2200 pF in series with the input


This is the best
so far...

- Higher coupling decreases loss slightly and gives loss margin at 30 MHz.
- Close wound has no visible effect
- The tape has no effect. 




49 to 1 Auto Transformer 140 mil wide Cu strip on 3T primary / 21T secondary
One FT240-52 Core

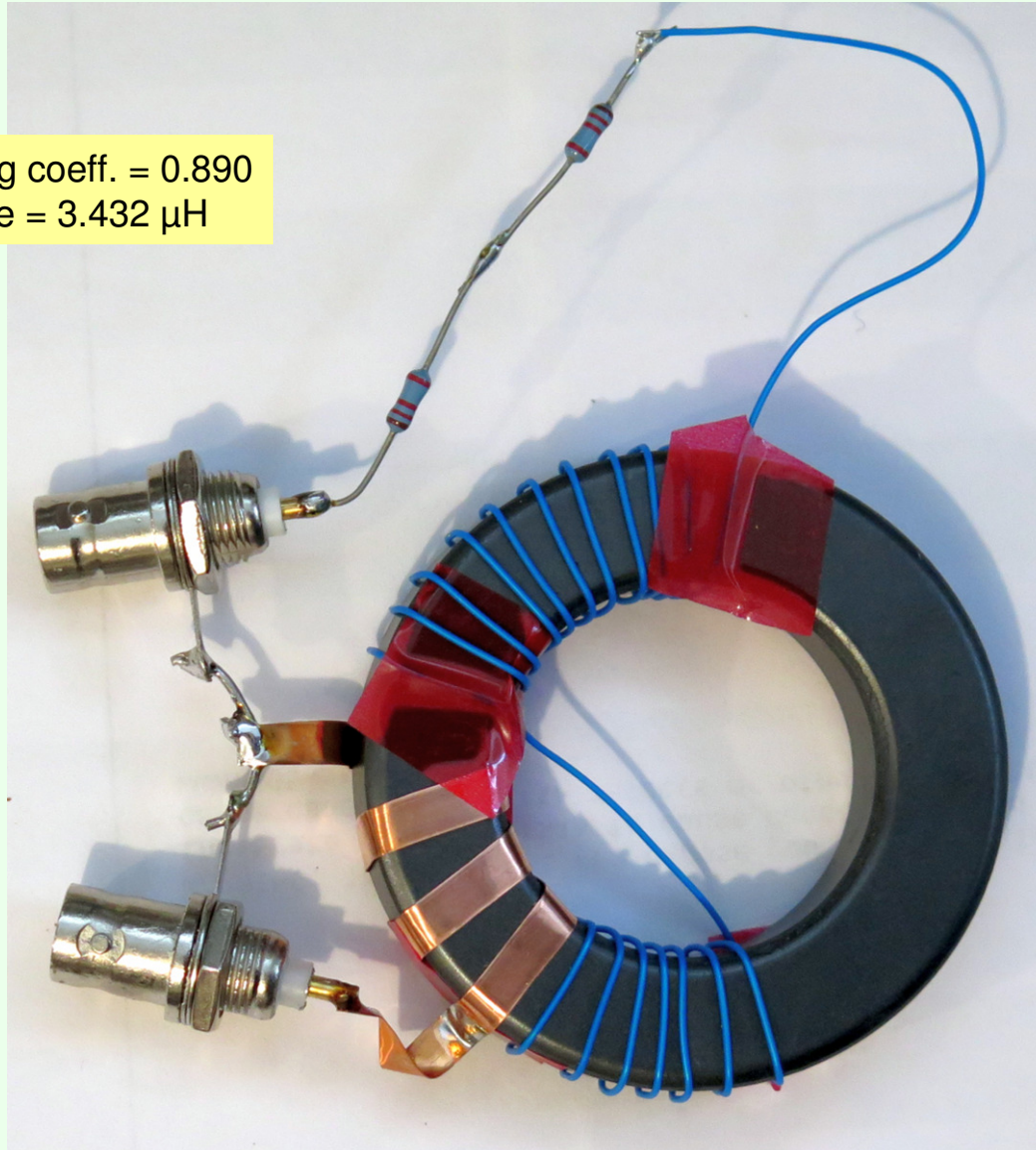Measured Coupling coeff. = 0.890
Primary Inductance = 3.432 μH



Added 80 pF Cap across input and
2200 pF in series with the input

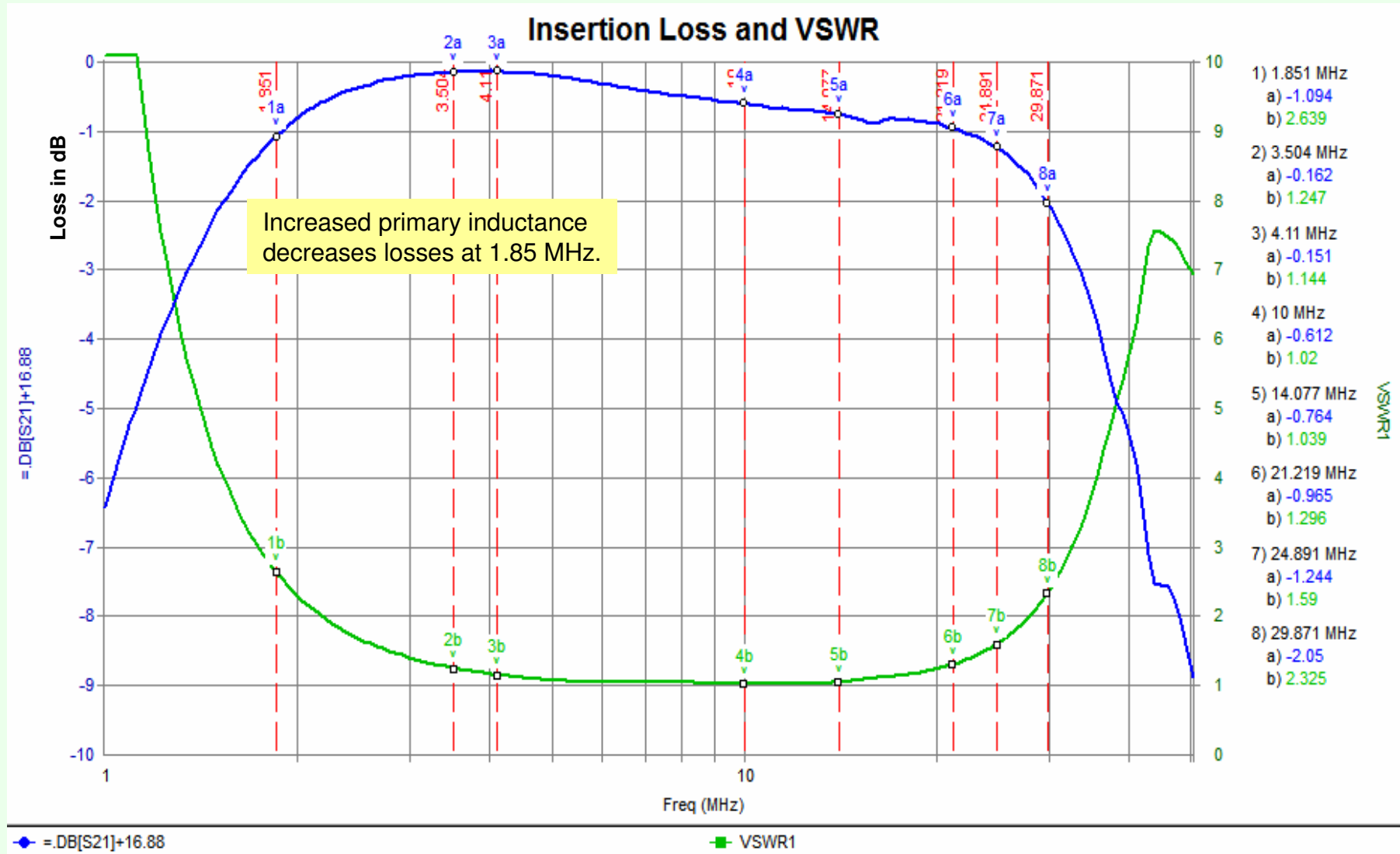Using one core increases losses
at the high end, since coupling is
reduced to 0.890



Ref: FT240-52-1cores-26wireVer3-NoCap-Tap-21a3Tours.wsp

49 to 1 Auto Transformer 140 mil wide Cu strip on 3T primary / 21T secondary
One FT240-52 Core Tight Winding

Measured Coupling coeff. = 0.949
Primary Inductance = 3.568 μH




49 to 1 Transformer 140 mil wide Cu strip on 3T primary / 21T secondary

One FT240-52 Core Tight Winding

Added 80 pF Cap across input and
2200 pF in series with the input


Good choice using
only one core

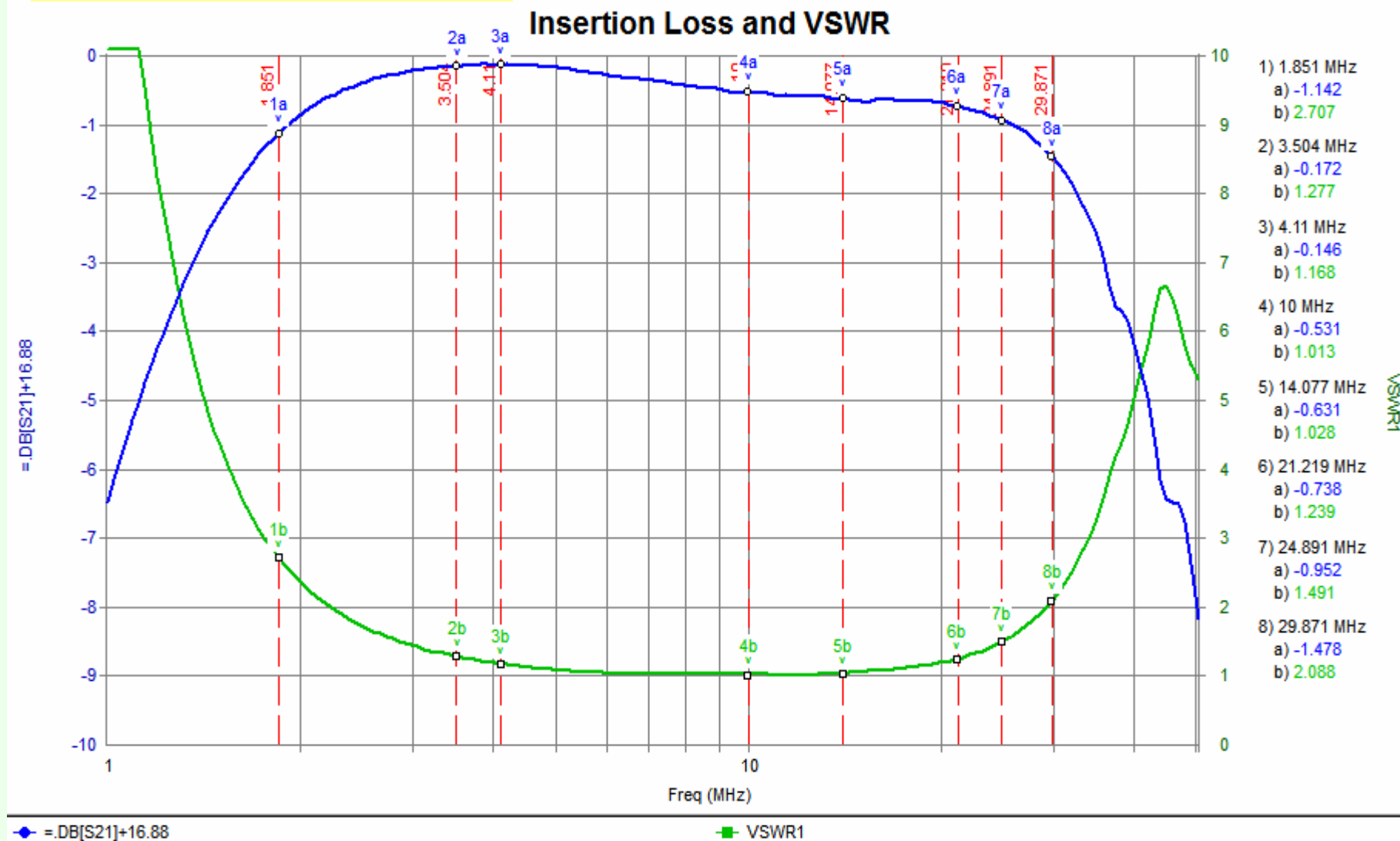Increased coupling gives...
Slight loss reduction above 20 MHz



49 to 1 Auto Transformer 140 mil wide Cu strip on 3T primary / 21T Total
Two FT240-52 Cores Tight Winding

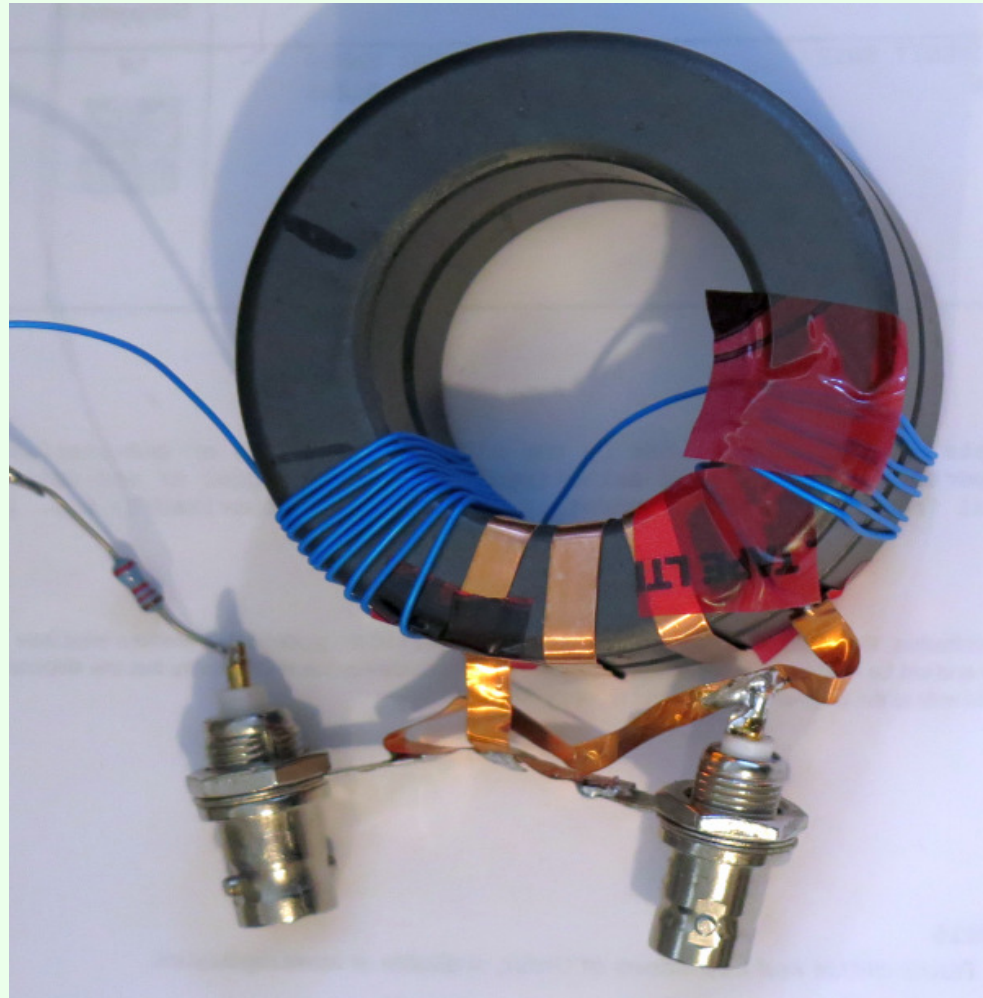Measured Coupling coeff. = 0.948
Primary Inductance = 6.919 μH




49 to 1 Transformer 140 mil wide Cu strip on 3T primary / 21T Total

Two FT240-52 Cores Tight Winding

Added 100 pF Cap across input and
2200 pF in series with the input


Increased coupling gives...

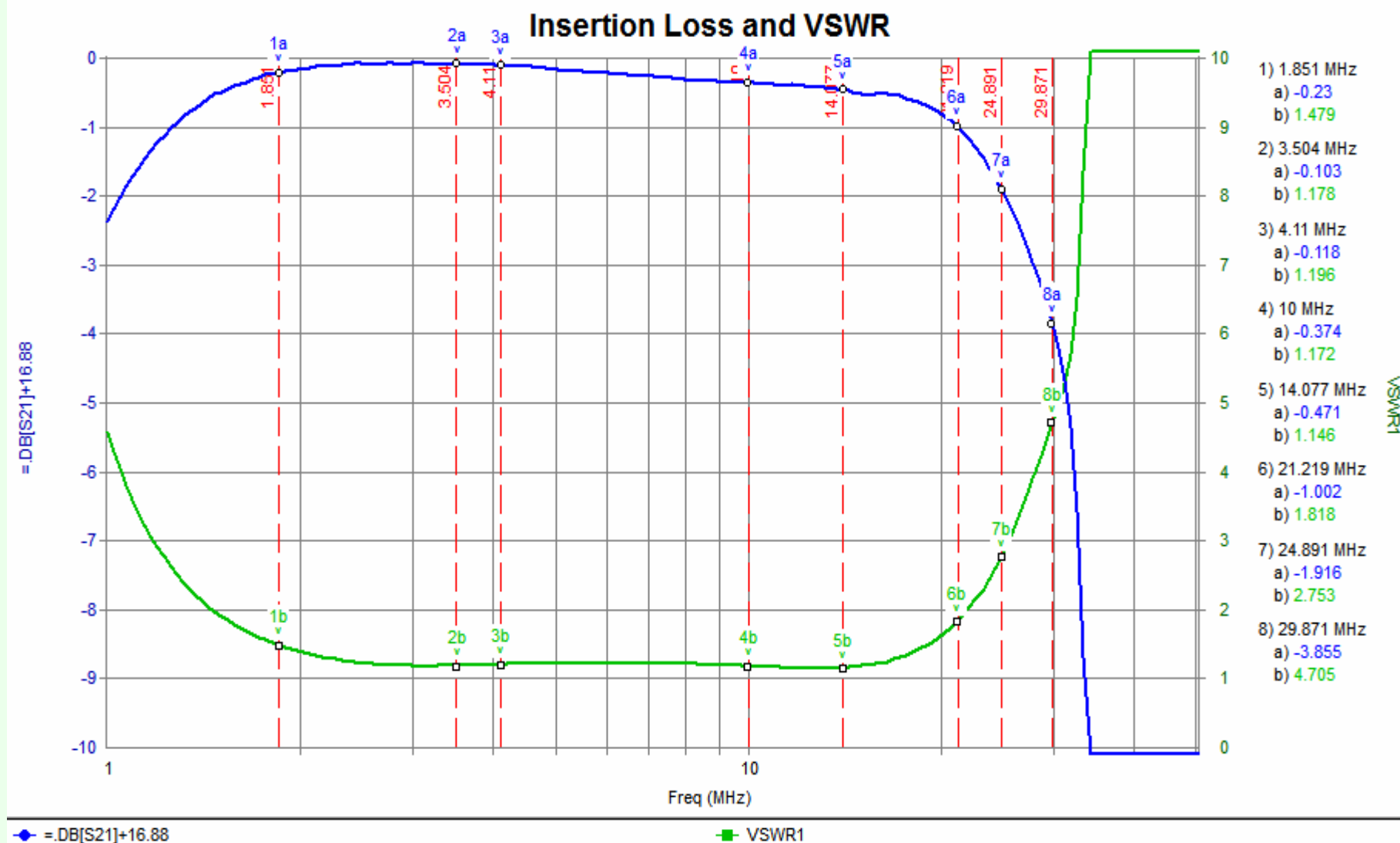- Much increased losses above 20 MHz coming from higher pri. inductance: not optimum
- But ... Low loss/VSWR on 160m



49 to 1 Transformer 140 mil wide Cu strip on 2T primary / 14T Secondary Two FT240-52 Cores Isolated Secondary Tight Winding

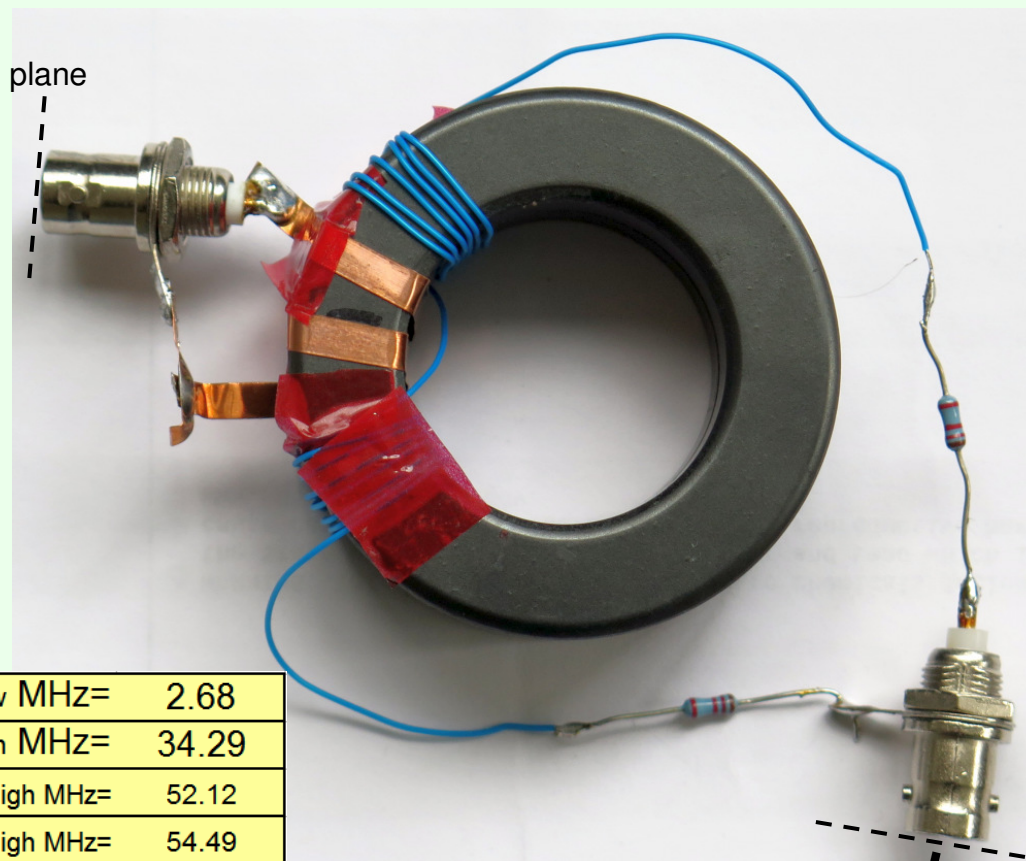Measured Coupling coeff. = 0.949
 Primary Inductance = 3.056 μ H



M = 19.26	Mutual inductance	F3 dB Low MHz=	2.68
K = 0.949	Coupling Coeff.	F3dB High MHz=	34.29
0.153	Primary leakage Inductance	F3dB High MHz=	52.12
7.156	Secondary leakage Inductan.	F3dB High MHz=	54.49

Ref.: Inductors M and K Calculations.xls

VNA
Port 2

High Isolation
HF Current Balun

8 in. BNC
cable

Cal plane


Ref.: <http://ve2azx.net/technical/ChokeCurrentBalun.pdf>

49 to 1 Transformer 140 mil wide Cu strip on 2T primary / 14T Secondary

Two FT240-52 Cores Isolated Secondary Tight Winding

Added 72 pF Cap across input and
2500 pF in series with the input

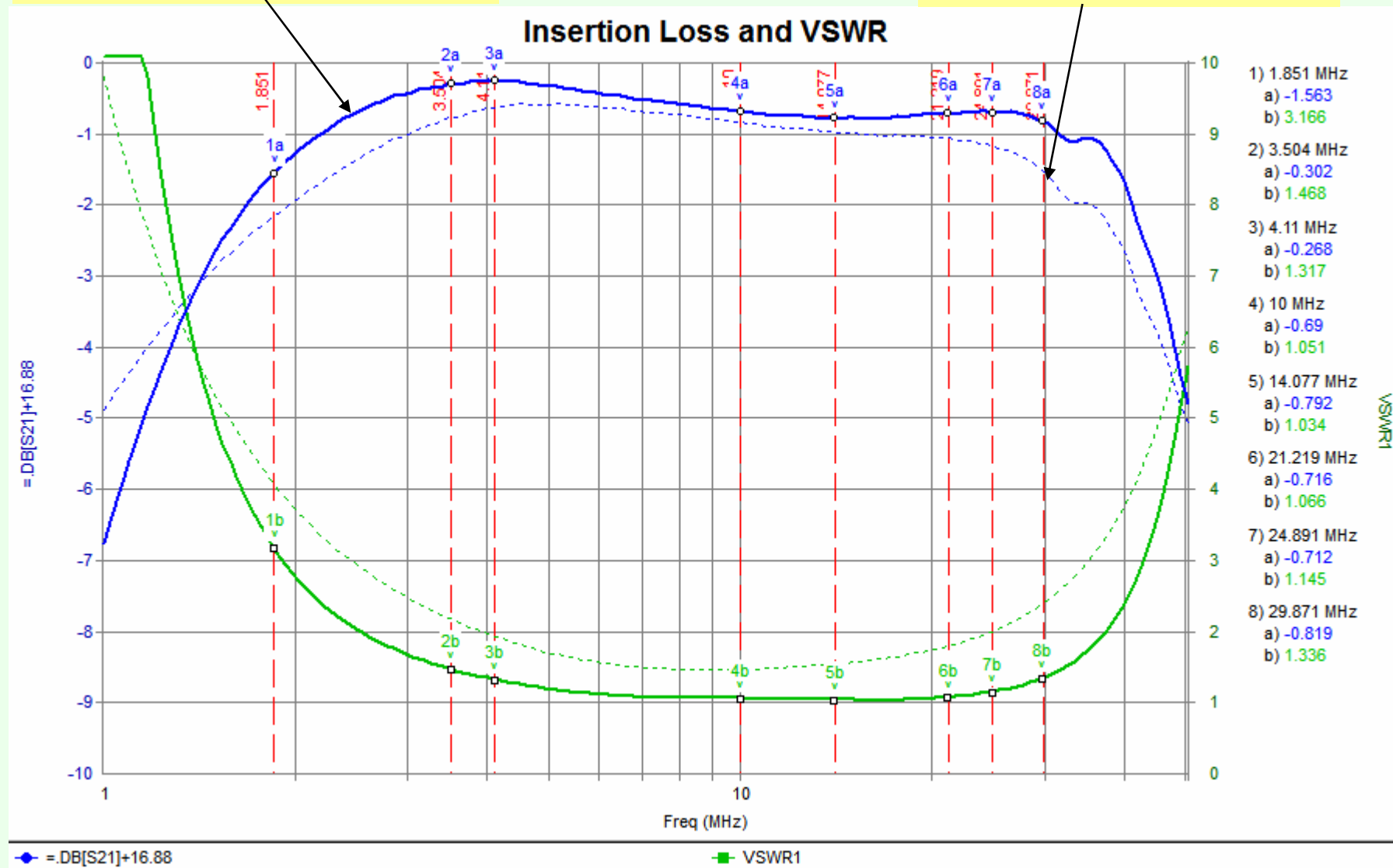No input cap across input and
No series cap at input




49 to 1 Transformer 140 mil wide Cu strip on 2T primary / 12T Secondary
Two FT240-52 Cores Isolated Secondary Tight Winding

This unit gave similar results as the 1:7 ratio version

49 to 1 Auto Transformer 140 mil wide Cu strip on 2T primary / 12T secondary
One Fair-Rite #2643251002 43 type Core


SPLIT SECONDARY

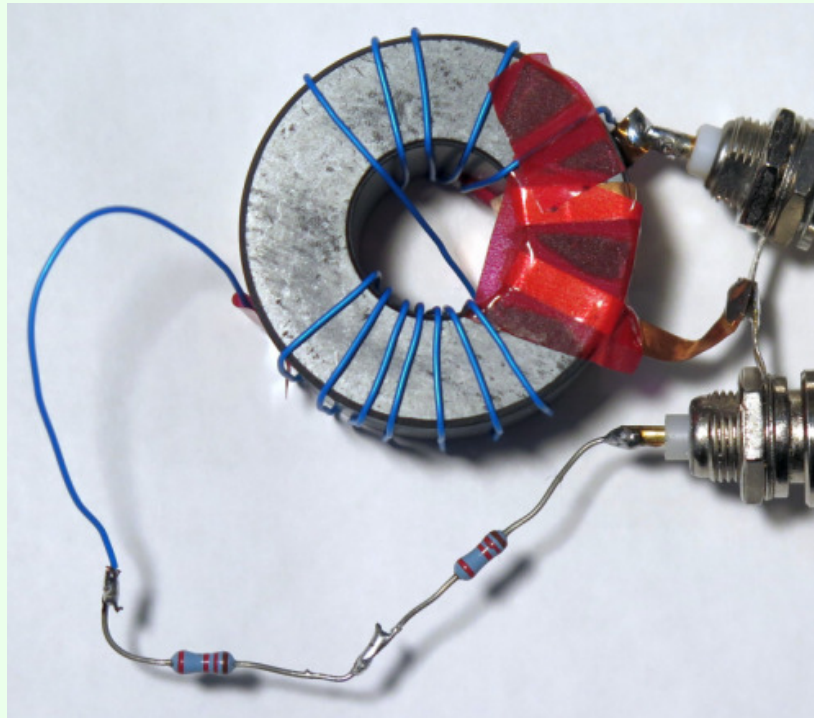

M = 75.23	Mutual inductance	F3 dB Low MHz=	0.62
K = 0.984	Coupling Coeff.	F3dB High MHz=	28.30
	0.209 Primary leakage Inductance	F3dB High MHz=	38.14
	7.417 Secondary leakage Inductan.	F3dB High MHz=	52.58


49 to 1 Auto Transformer 140 mil wide Cu strip on 2T primary / 12T secondary One Fair-Rite #2643251002 43 type Core

Added 100 pF Cap across input

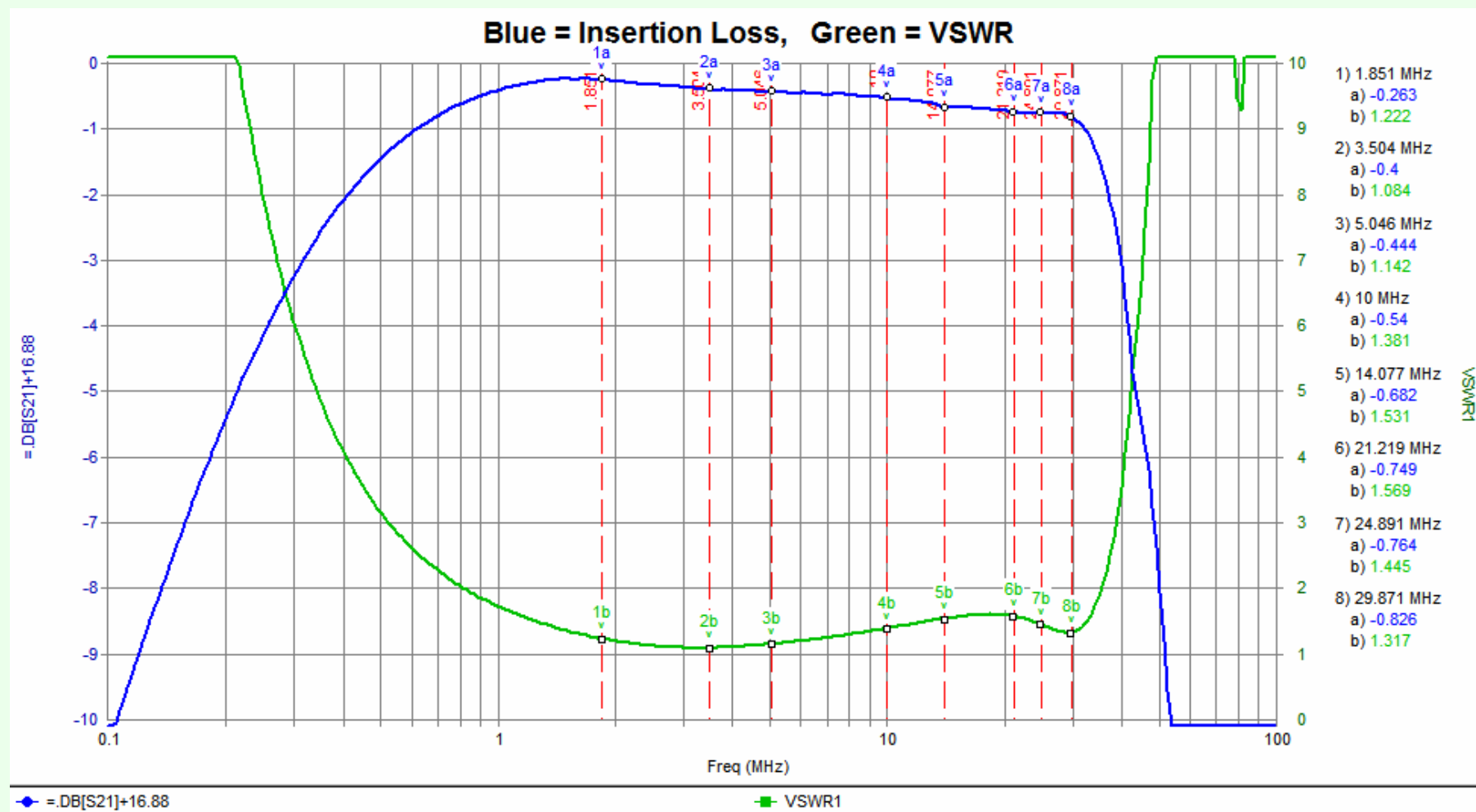


49 to 1 Auto Transformer 140 mil wide Cu strip on 2T primary / 12T secondary One Fair-Rite #2643251002 43 type Core

Added 100 pF Cap across input

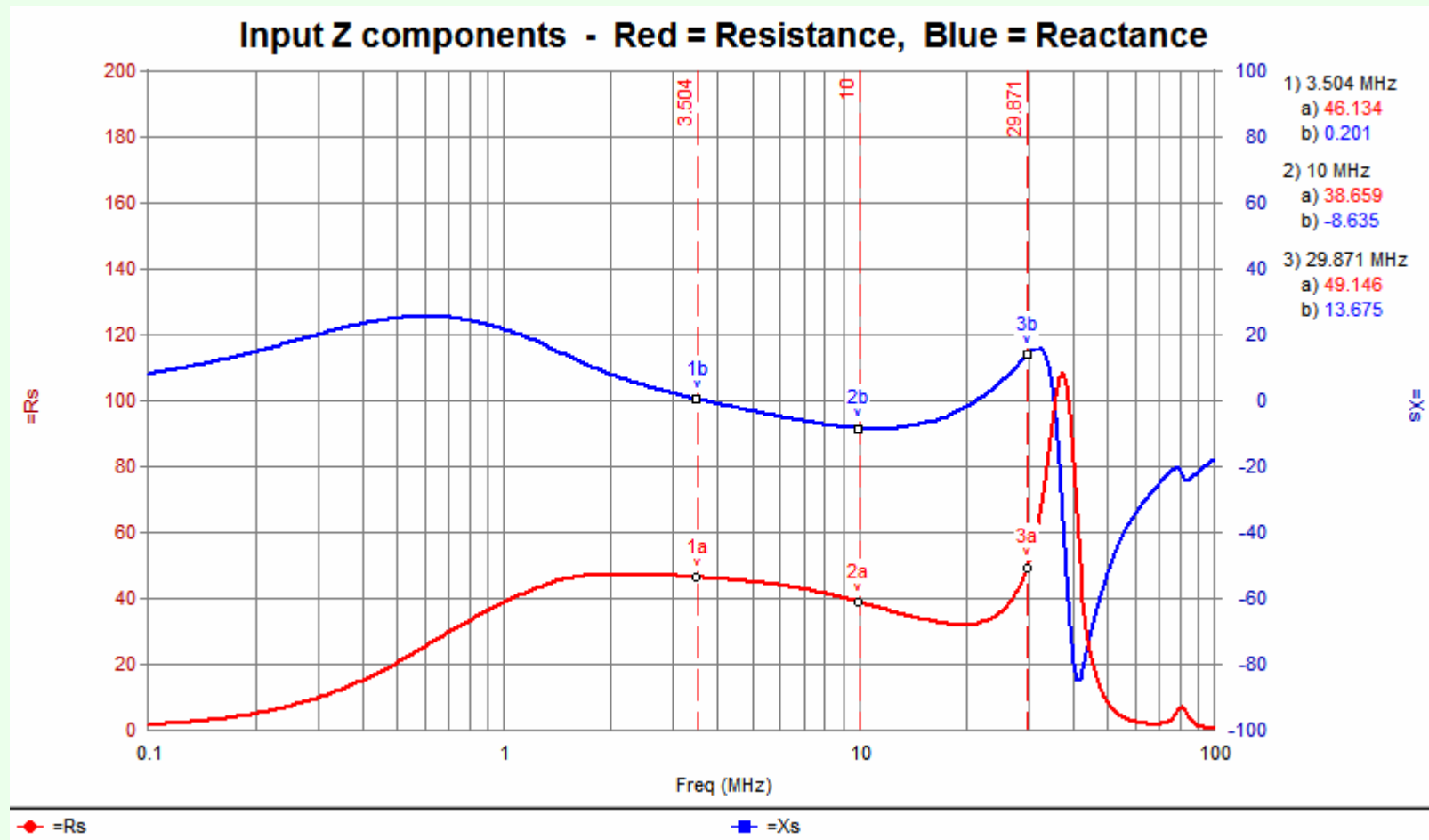

49 to 1 Auto Transformer 140 mil wide Cu strip on 2T primary / 12T secondary
One Fair-Rite #2643251002 43 type Core

CONTINUOUS SECONDARY

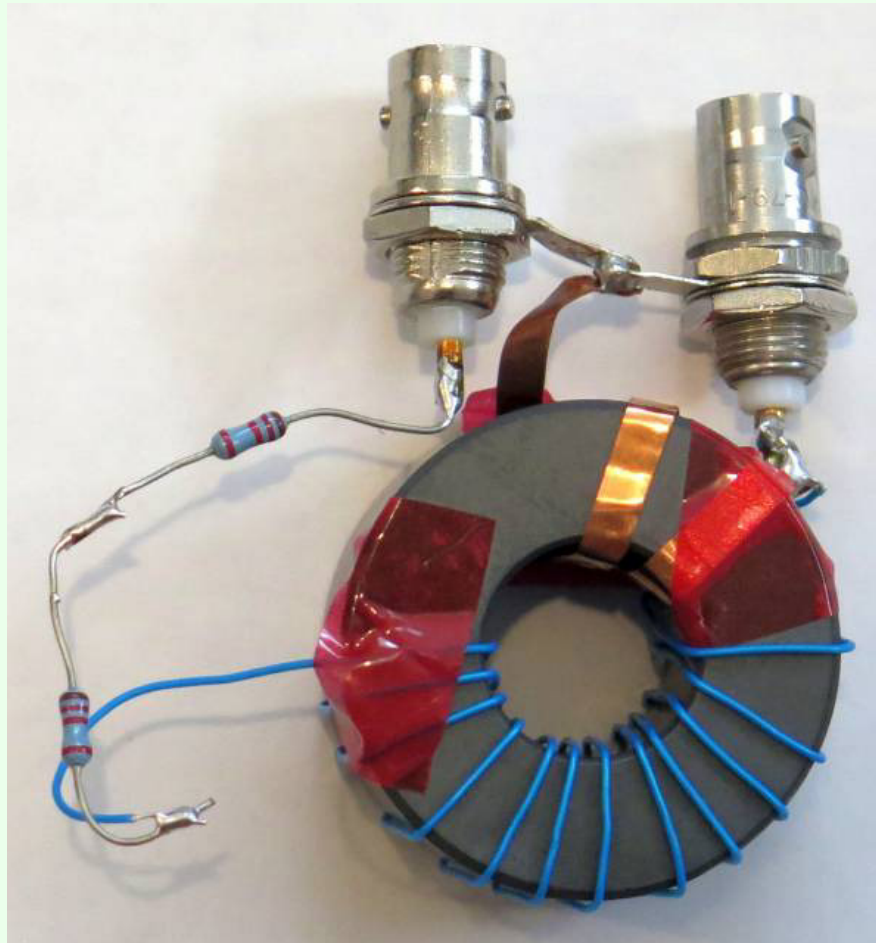


M = 74.28	Mutual inductance	F3 dB Low MHz= 0.63
K = 0.980	Coupling Coeff.	F3dB High MHz= 22.75
0.259	Primary leakage Inductance	F3dB High MHz= 30.68
9.239	Secondary leakage Inductan.	F3dB High MHz= 42.21


49 to 1 Auto Transformer 140 mil wide Cu strip on 2T primary / 12T secondary One Fair-Rite #2643251002 43 type Core

Added 100 pF Cap across input

CONTINUOUS SECONDARY

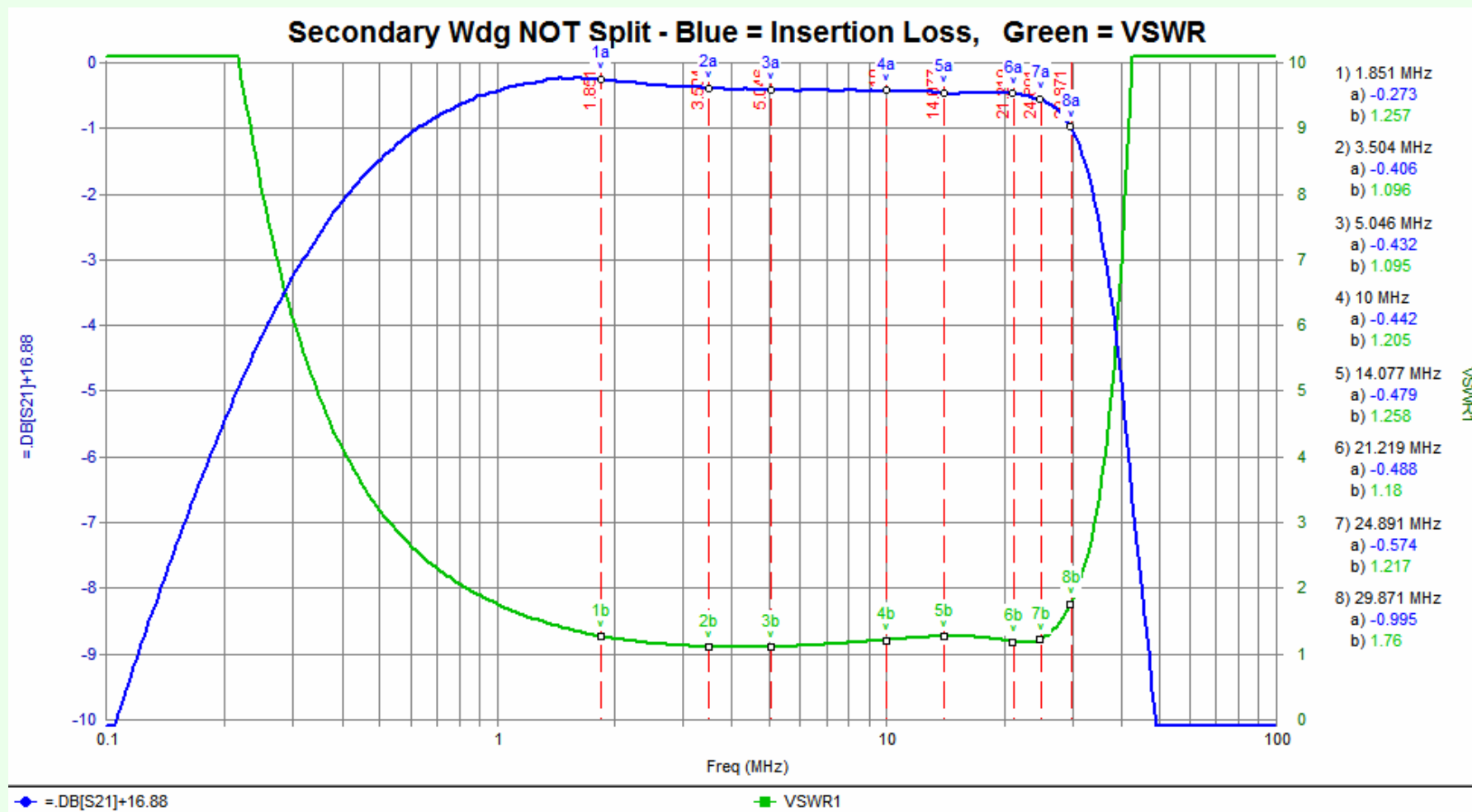

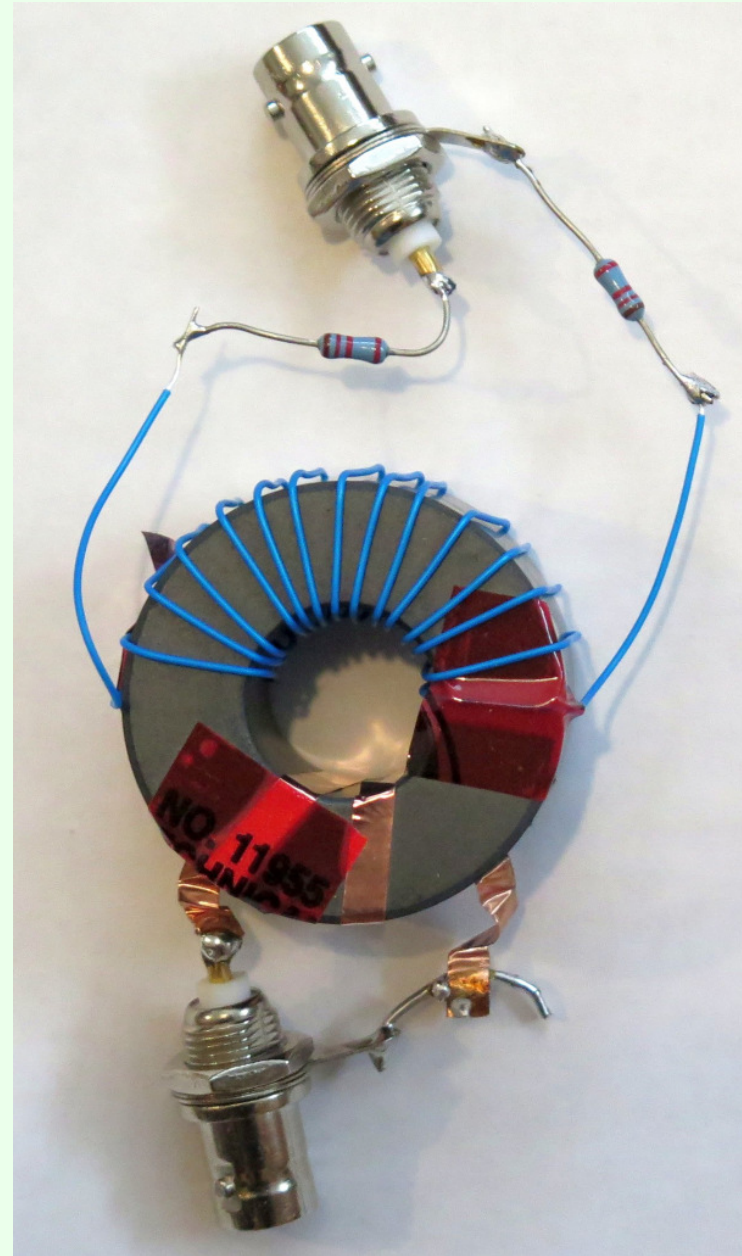49 to 1 Transformer Floating Output
140 mil wide Cu strip on 2T primary / 14T secondary
One Fair-Rite #2643251002 43 type Core




49 to 1 Transformer Floating Output

140 mil wide Cu strip on 2T primary / 14T secondary


One Fair-Rite #2643251002 43 type Core

Added 100 pF Cap across input

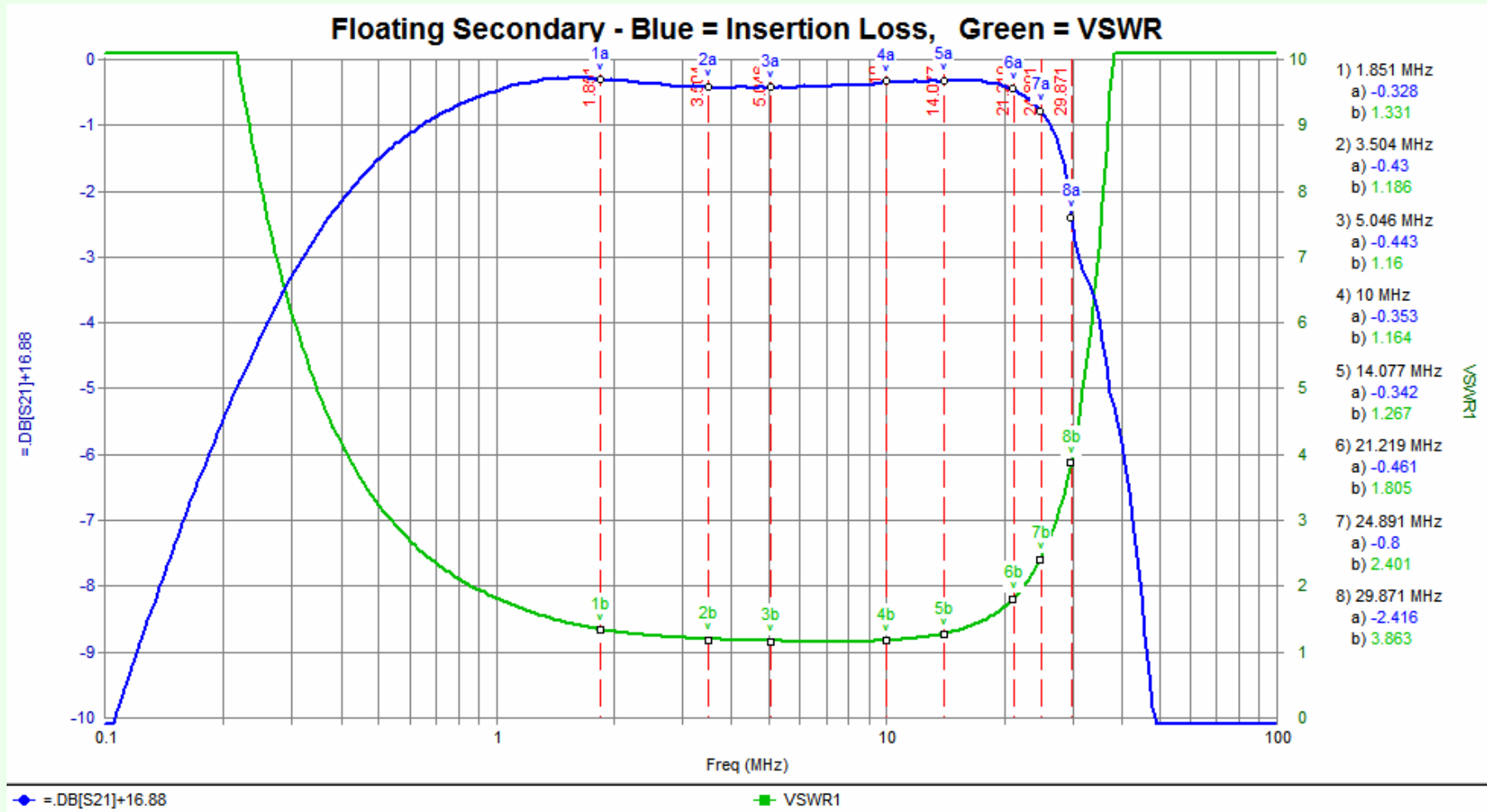

49 to 1 Transformer Floating Output - Divided Secondary
140 mil wide Cu strip on 2T primary / 14T secondary
One Fair-Rite #2643251002 43 type Core

Added 100 pF Cap across input

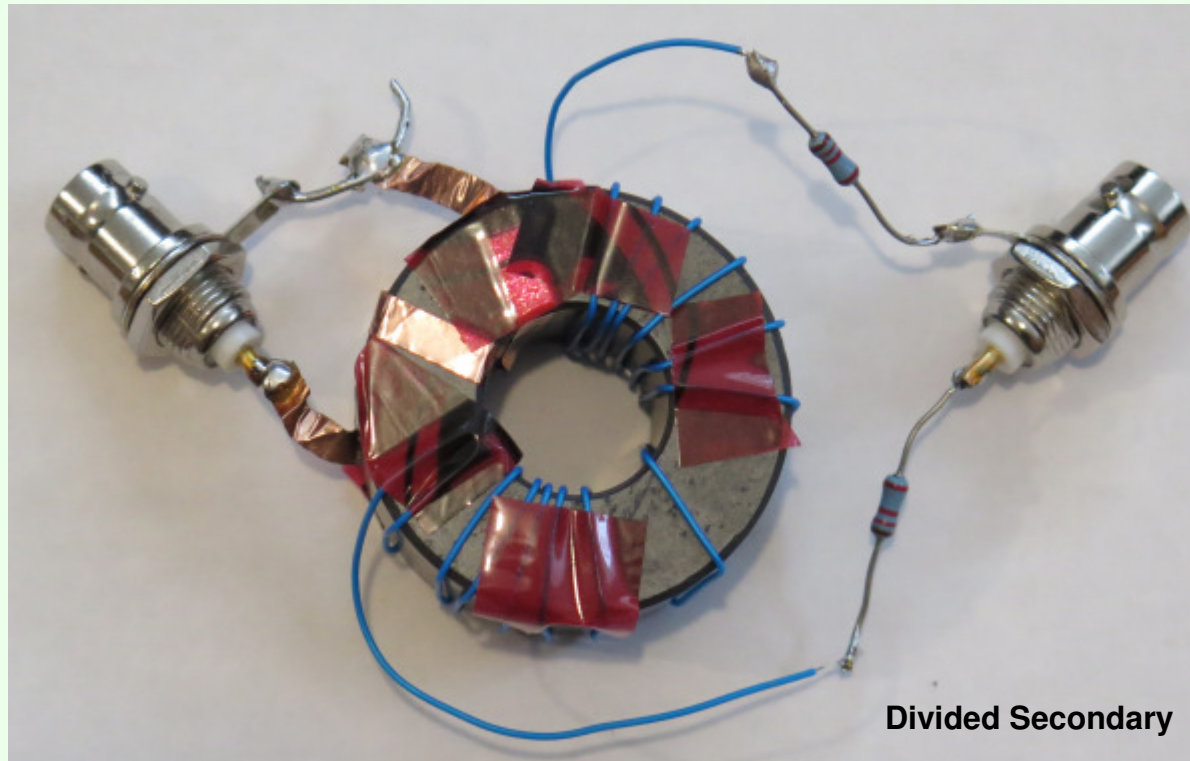


M = 87.30	Mutual inductance	F3 dB Low MHz= 0.63
K = 0.987	Coupling Coeff.	F3dB High MHz= 32.03
0.161	Primary leakage Inductance	F3dB High MHz= 49.45
7.784	Secondary leakage Inductan.	F3dB High MHz= 50.09

49 to 1 Transformer Floating Output - Divided Secondary

140 mil wide Cu strip on 2T primary / 14T secondary

One Fair-Rite #2643251002 43 type Core

Added 100 pF Cap across input

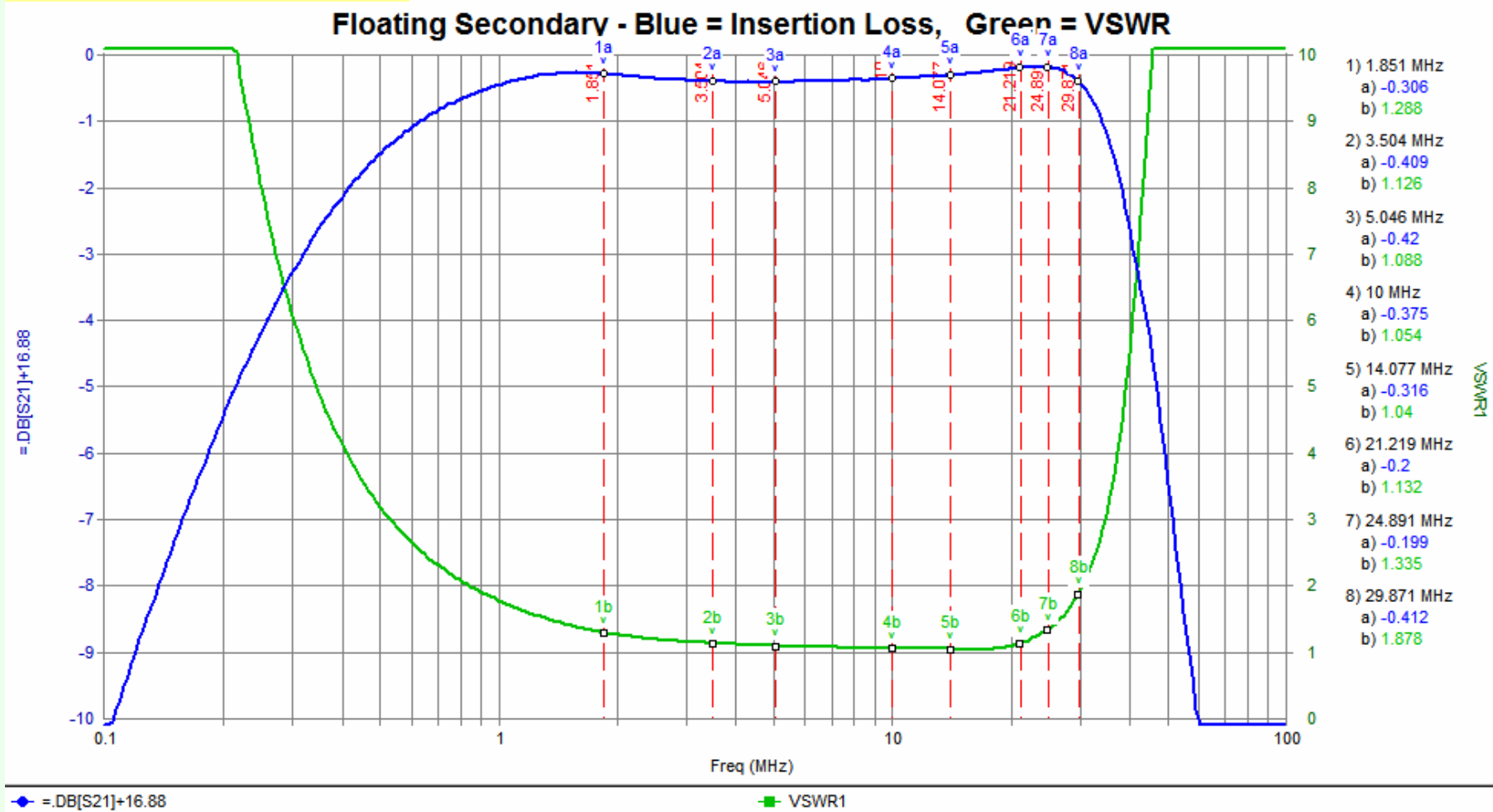

49 to 1 Transformer Floating Output - Divided Secondary


140 mil wide Cu strip on 3T primary / 21T secondary

One Fair-Rite #2643251002 43 type Core

Added 100 pF Cap across input

Since the maximum power is proportional to the number of turns squared,
 Why not use a 3 to 21 turns ratio ?
 Going from 2T to 3T on the primary should increase the maximum power by:
 $(3/2)^2 = 2.25$ times
 Ref: Inductors M and K Calculations.xls / Core Max Power

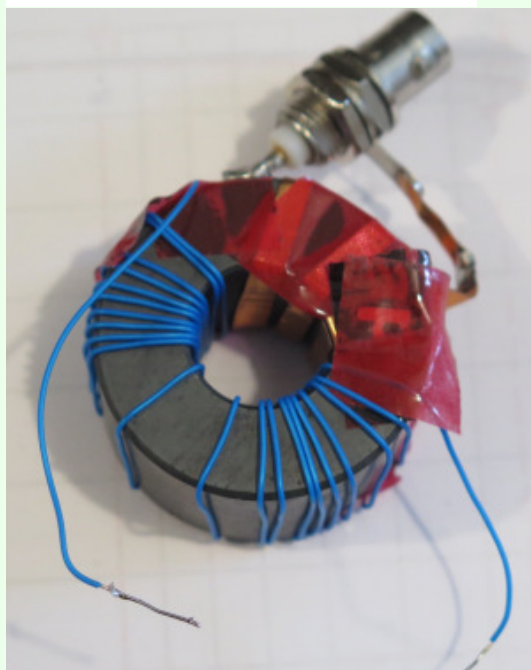Fair-Rite core #2643251002
 1.54 x 0.66 x .875 in.
 43 material $\mu = 800$



Note that the coupling coefficient is close to 1.

M = 200.15	Mutual inductance	F3 dB Low MHz=	0.28
K = 0.993	Coupling Coeff.	F3dB High MHz=	25.66
	0.201 Primary leakage Inductance	F3dB High MHz=	39.69
	9.738 Secondary leakage Inductan.	F3dB High MHz=	40.04


49 to 1 Transformer Floating Output - Divided Secondary

140 mil wide Cu strip on 3T primary / 21T secondary


One Fair-Rite #2643251002 43 type Core

Added 53 pF Cap across input

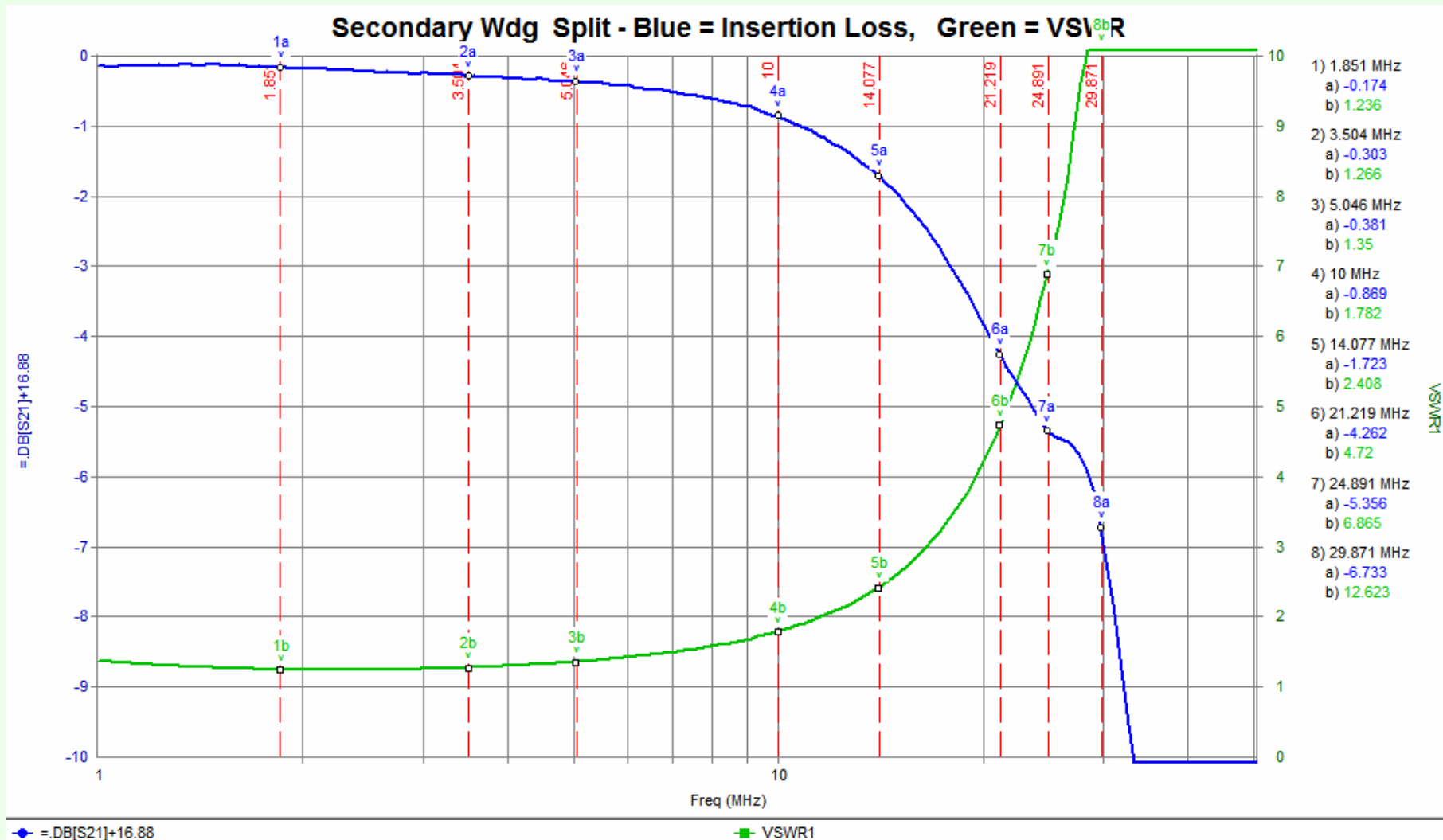Too much losses above 10 MHz,
even if coupling coeff. is close to unity.
BUT Low frequency performance
extends far below 1 MHz



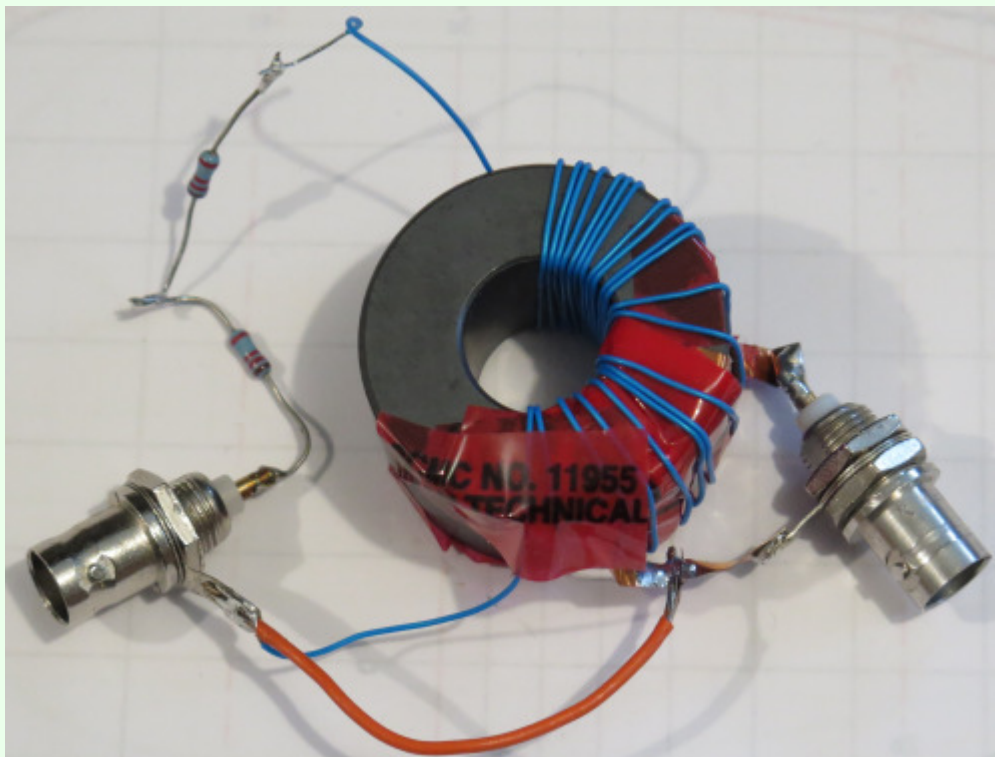49 to 1 Transformer Floating Output - Secondary wound over Primary
140 mil wide Cu strip on 3T primary / 21T secondary
Prim and Sec interconnected. Tape added over the primary.
One Fair-Rite #2643251002 43 type Core




With Sec. wound over the Prim.,
the coupling factor is very close to 1

M = 202.30	Mutual inductance	F3 dB Low MHz= 0.28
K = 1.003	Coupling Coeff.	F3dB High MHz= 56.93
-0.090	Primary leakage Inductance	F3dB High MHz= -88.14
-4.393	Secondary leakage Inductan.	F3dB High MHz= -88.76

49 to 1 Transformer Floating Output - Secondary wound over Primary 140 mil wide Cu strip on 3T primary / 21T secondary Prim and Sec interconnected. Tape added over the primary. One Fair-Rite #2643251002 43 type Core


Added 100 pF Cap across input

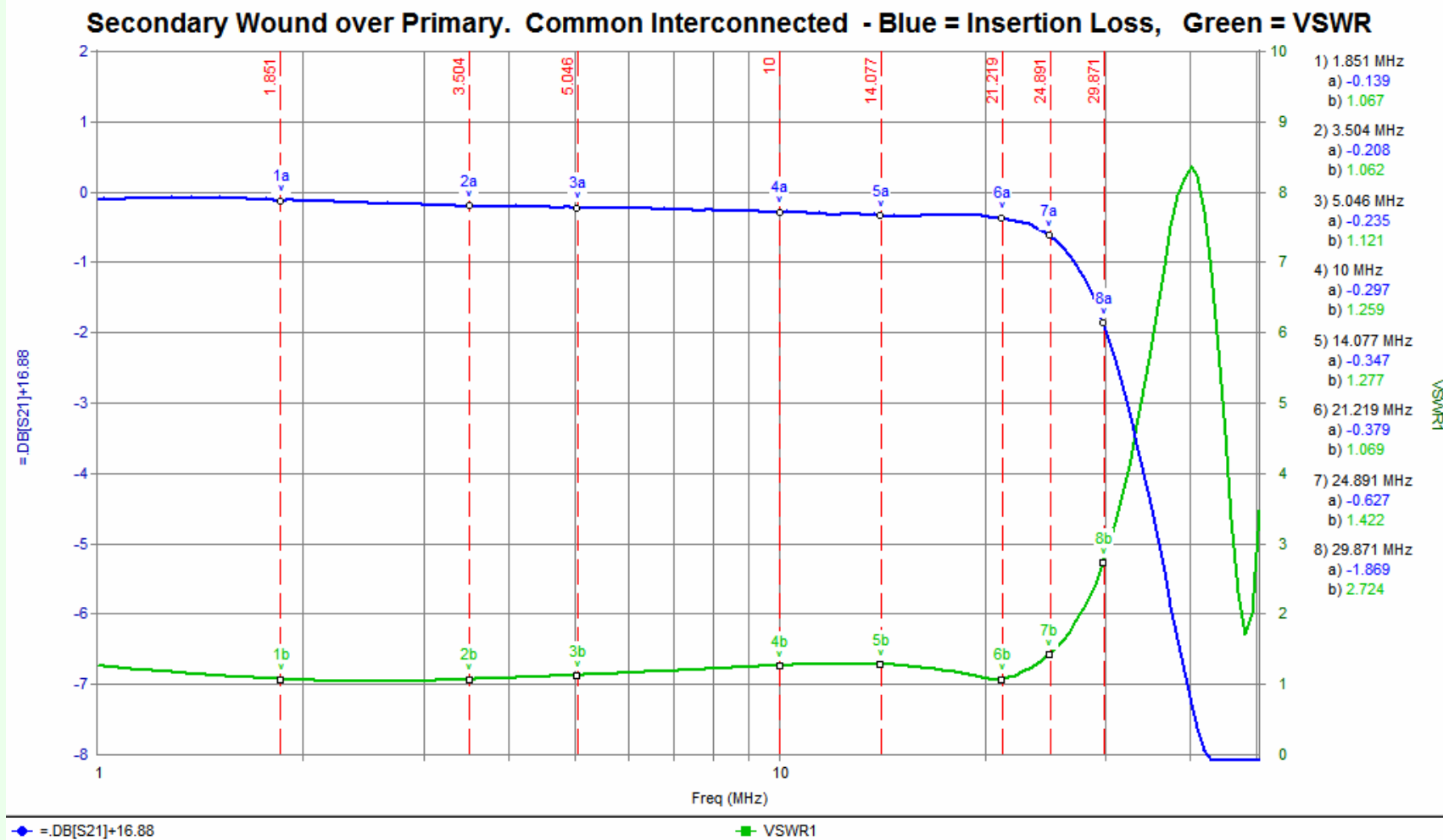- With Sec. wound over the Prim., the coupling factor is very close to 1
- Response OK up to 25 MHz.
- Low freq. performance has shifted towards low frequencies
Only 0.14 dB loss at 1.8 MHz



Modelling the 49 to 1 UNUN


separate primary/secondary model

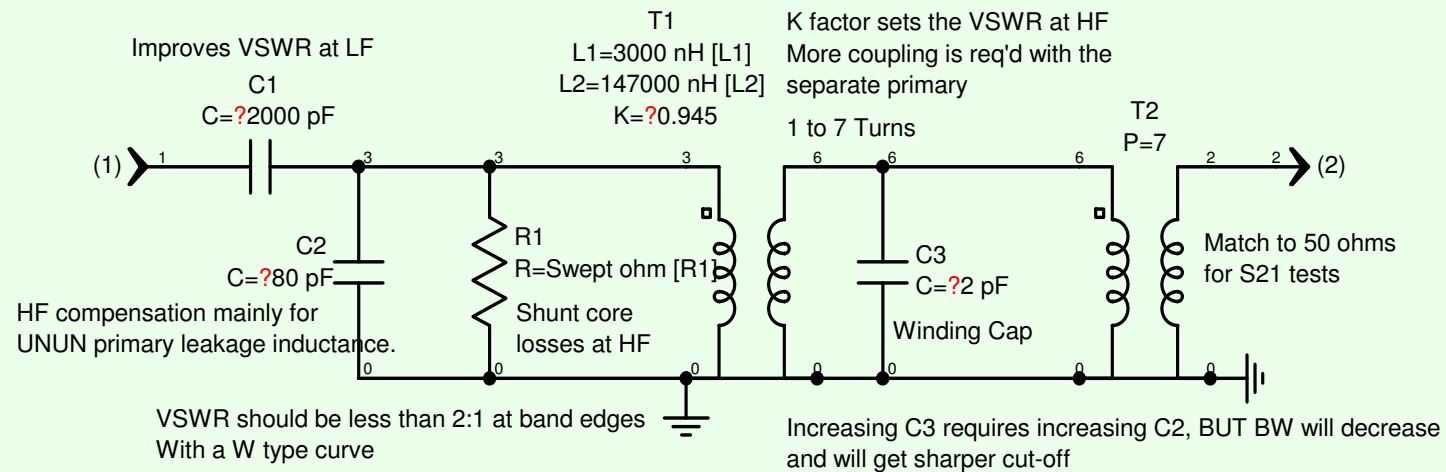

R1 vs FREQ modelled from:
FT240-52-2cores-2T-CuStrip-Ver2-PrimaryOnly-Sec26wireOpen.wsp
and: FT240-52-2cores-2T-CuStrip-Ver2-PrimaryOnly-Sec26wireOpen.xls
R1 decreases at higher freq causing increased losses

Ref: Transformer_sim3_FT240-52-R1_modelled.wsp

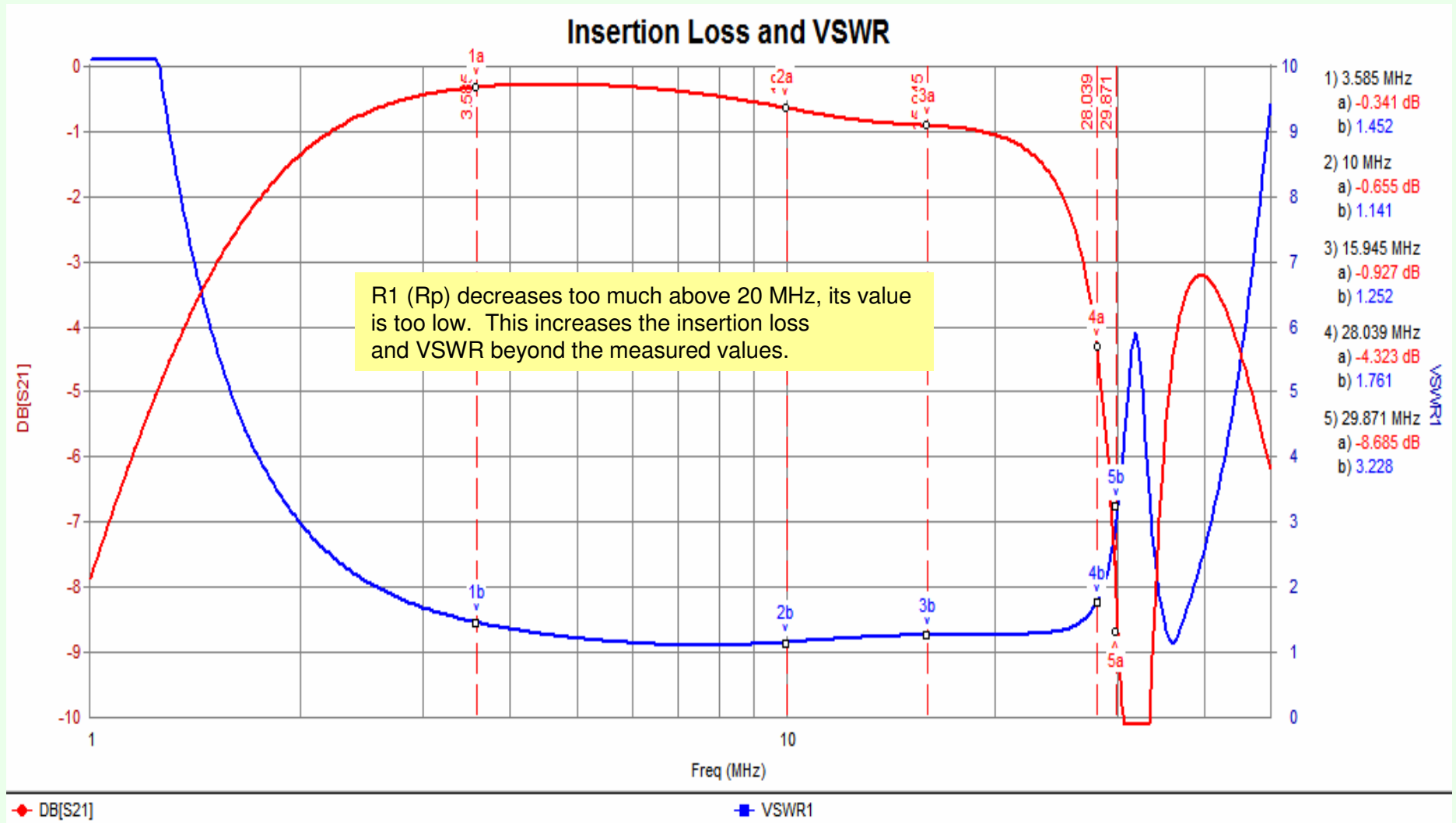Using the measured R1 (parallel Rp) with open secondary in the previous model





Ref: Transformer_sim3_FT240-52-R1_modelled.wsp

Simulations of Tapped Inductor/Transformer


Increasing primary inductance L1:

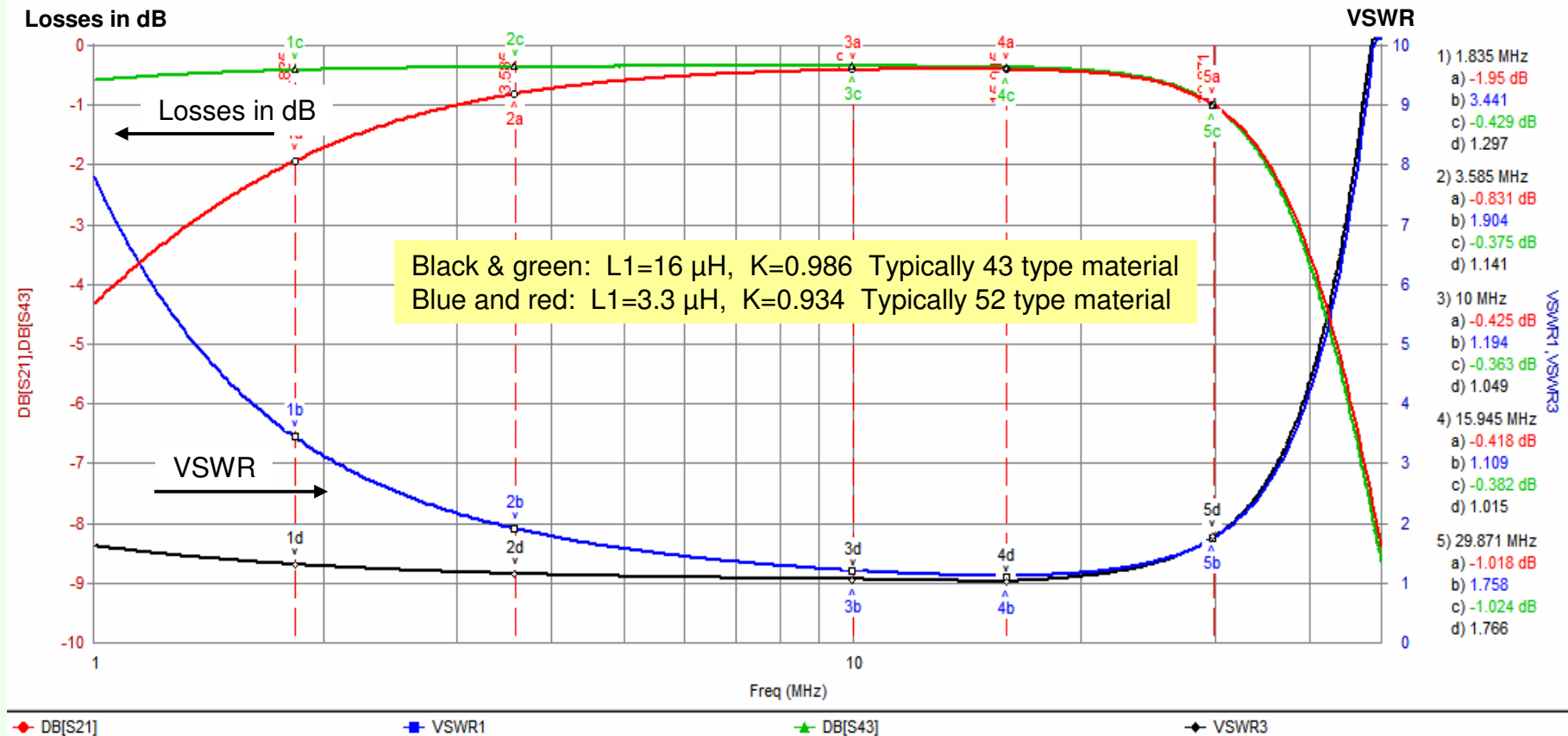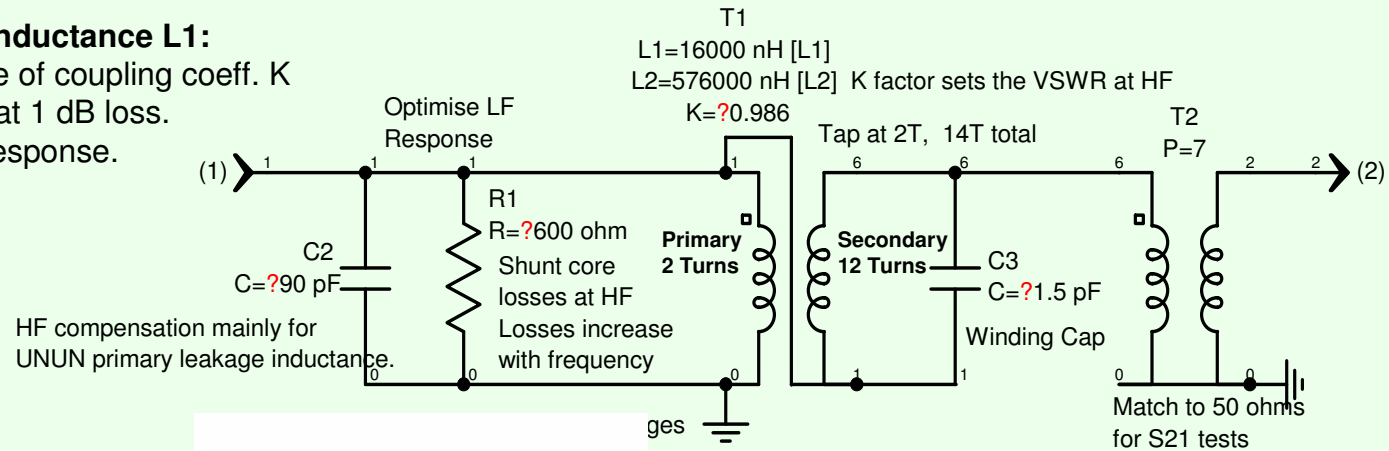- Requires an increase of coupling coeff. K
- to keep HF response at 1 dB loss.
- Improves low freq. response.



Simulations of Tapped Inductor

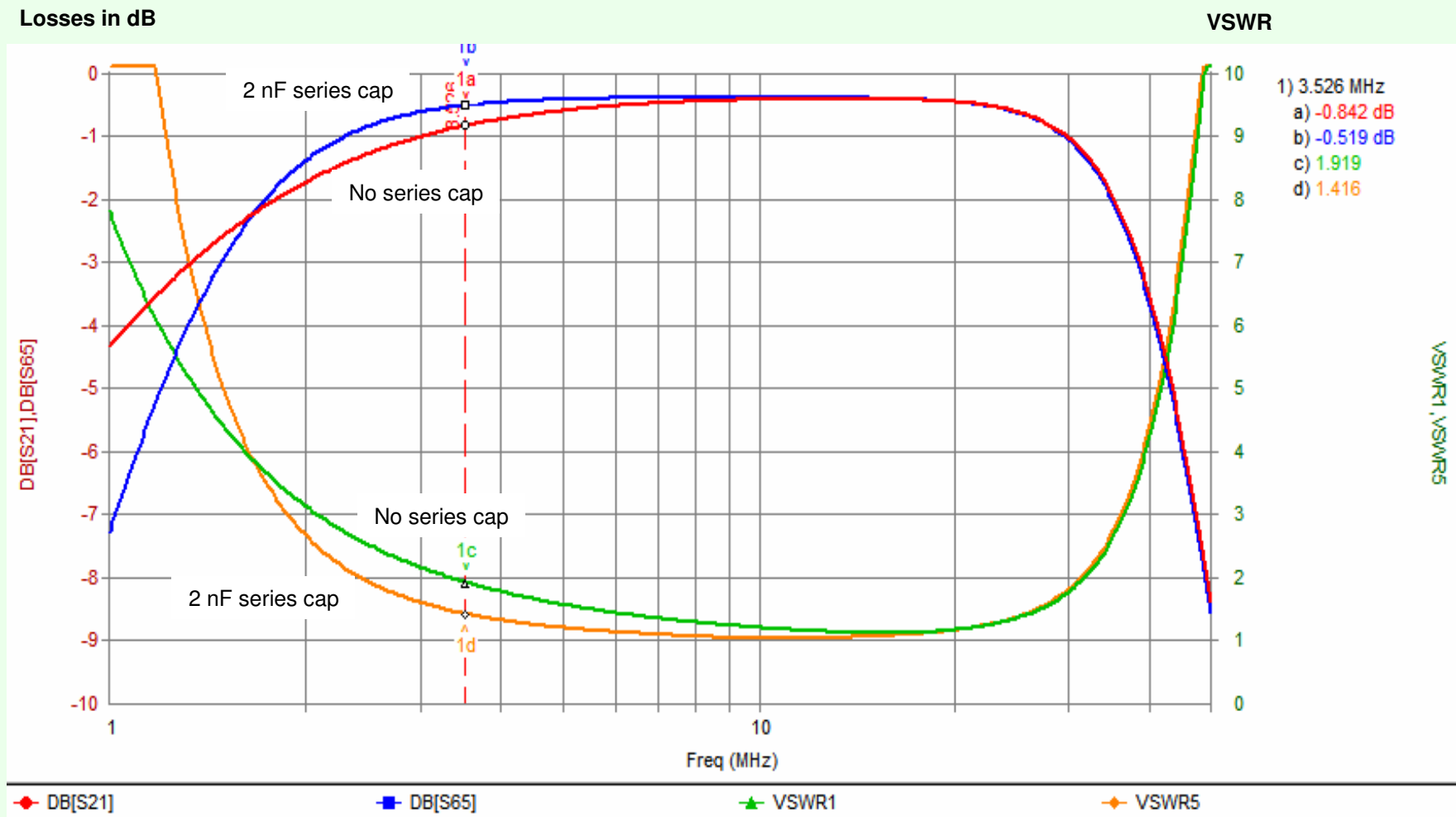Series Capacitor improves Losses and VSWR at low frequencies



Adding a shunt Inductor before the Series Capacitor

(pink and brown) Allows coverage of 160m band.

